

# ECE 485 Project #2

Jay Mundrawala

November 23, 2009

## Abstract

This project describes the design and implementation of a multicycle MIPS datapath. Along with it are testbenches that issue the appropriate signals for a few signals.

## 1 Introduction

The goal of this project was to implement a MIPS datapath capable of executing a small set of instructions. For this project, we were to implement the following instructions:

- LW
- SW
- ADD
- SUB
- AND
- OR
- SLT
- BEQ
- J
- BNE
- ADDI
- SLL
- LUI
- JAL

The source code for this datapath is available in the appendix and in a git repository on github. This is available at [http://github.com/whois/ECE485\\_P2](http://github.com/whois/ECE485_P2).

## 2 Design

The design for a multicycle MIPS datapath is quite simple. It is shown in Figure 1. The data path has the following signals coming from the control unit, which describe how the datapath should operate: PCWrite, IorD, MemRead, MemWrite, IRWrite, RegDst, MemToReg, RegWrite, ALUSrcA, ALUSrcB, ALUOp, and PCSrc. Tables 1 through 6 enumerate the possible values for these signals and Listings 19 contains their definitions.

Signal name	Effect when deasserted	Effect when asserted
PCWrite	None	PC is written
PCWriteCondEq	None	PC is written if zero is asserted
PCWriteCondNEq	None	PC is written if zero is deasserted
IorD	Instruction is Fetched	Data is fetched
MemRead	None	Memory at given address is read
MemWrite	None	Data is written to given address
IRWrite	None	Instruction register is written
RegWrite	None	Data is written to register
ALUSrcA	Port A of ALU gets PC	Port A of ALU gets register A's output

Table 1: Actions of 1-bit control signals

ALUSrcB	
Signal value	Effect
ASB_REGB	Port B of ALU gets register B's output
ASB_FOUR	Port B of ALU gets 4
ASB_SEXT	Port B of ALU gets instruction[15-0] sign extended to 32 bits
ASB_SEXTS	Same as previous except value is shifted left by 2

Table 2: Actions of ALUSrcB signal

ALUOp	
Signal value	Effect
AOP_AND	ALU will 'and' the two operands
AOP_OR	ALU will 'or' the two operands
AOP_ADD	ALU will add the two operands
AOP_SUB	ALU will subtract A - B
AOP_SLT	ALU will output '1' if $A < B$ , '0' otherwise
AOP_NOR	ALU will NOR the two operands
AOP_SLL	ALU will shift B left by instruction[10-6]

Table 3: Actions of ALUOp signal

With these signals defined, we can begin by defining each functional block in Figure 1. First, we have the PC. This is the program counter and stores the address of the next instruction to be executed. The memory block is our RAM. For this project, the test benches only output one value when the memory is read, and that is the instruction we are testing. This allows us to test the datapath without creating a memory module. Nothing is ever written to the memory; when testing LW we analyze the value on the

PCSource	
Signal value	Effect
PS_PCINC	Value to PC is $PC + 4$
PS_ALUOUT	Value to PC is that of the register ALU OUT
PS_JMP	Value to PC is $PC[31 - 28] + Instr[25 - 0] < 2$

Table 4: Actions of PCSource signal

RegDst	
Signal value	Effect
RD_RT	Write register is set to $instr[25-21]$
RD_RD	Write register is set to $instr[20-16]$
RD_RA	Write register is set to $R31$

Table 5: Actions of RegDst signal

write data line when it is time to write to the memory. The instruction register holds the values of the instruction being executed. The memory data register(MDR), stores the value read from memory. This will be written every clock cycle since the value only need be stored for one clock cycle. Thus, it does not need its own control signal and its enable can be attached to the clock. The register file, denoted by Registers in Figure 1, stores the 32 registers. Register A and B store the output of the register file for one clock cycle. The ALU does all the arithmetic computations. Its functionality is fully described by Table 3. The ALU OUT register holds the output of the ALU for one clock cycle. PCWrite Generate generates the enable signal to write to the PC. In the case of this design, it is described by the following equation:  $G = PCWrite + PCWriteCondEq * zero + PCWriteCondNEq * \overline{zero}$ .

## 2.1 Instruction Fetch, Instruction Decode, and Branch Target Computation

There are two steps that each instruction execution has in common. The first is the IF stage. Each instruction needs to be fetched from memory. To do this, we need to read the instruction from memory and store it into the instruction register. This is also the step where we must update the PC to  $PC + 4$ . So, with that in mind, we can define the signals needed to complete this step. First, IorD needs to be deasserted. This will select the PC as the address for memory. MemRead needs to be set, so that the instruction is fetched from memory. IRWrite needs to be asserted so that the instruction is stored after it is read. This is enough to actually fetch the instruction, but the PC still needs to be updated. Thus, we require ALUSrcA to be deasserted to select PC for port A of the ALU, and ALUSrcB to be set to ASB.FOUR to select 4 for the second port( $PC + 4$ ). PCSource needs to be set to PS\_PCINC indicating that  $PC + 4$  should be written to the PC. Finally, PCWrite needs to be asserted so that the value is written to the PC. One thing that should be noted is that all writes happen only when the clock is high, except for the IRWrite. This is a bug, however it does not affect the system in any way.

The next step is the instruction decode stage. In this stage, we do two things. First, we read the registers from the register file. This is done automatically by the instruction register. Since the ALU is not being used in this stage, its a good time to calculate the

MemToReg	
Signal value	Effect
MTR_ALUOUT	Register write data gets the output of the ALU OUT register
MTR_MDR	Register write data gets the output of the MDR register
MTR_PC	Register write data gets the PC

Table 6: Actions of MemToReg signal

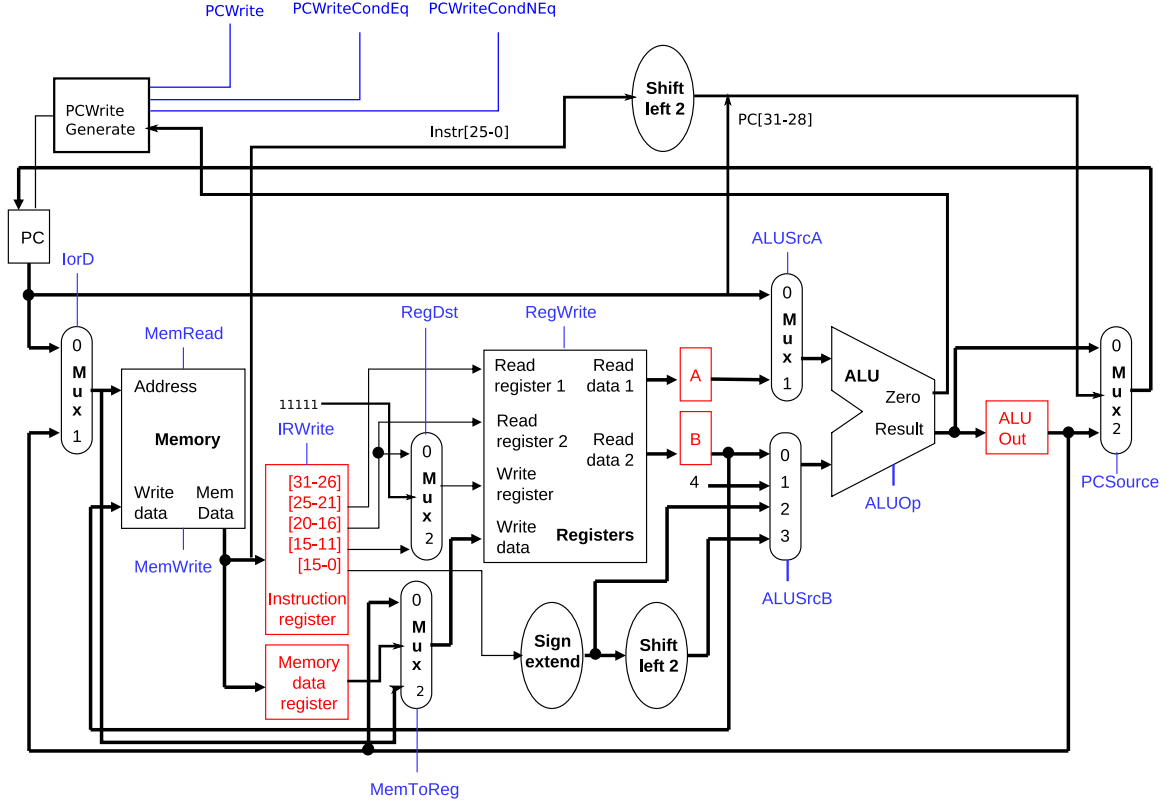


Figure 1: MIPS multicycle datapath

branch target address, regardless of if the instruction is a branch or not. This way, the target is ready incase it is a branch instruction. To do this, ALUSrcA is deasserted, indicating port A of the ALU gets the value of the PC. ALUSrcB is set to indicate the sign extended and shifted value of instruction[15-0]. These two will be added and stored in ALU OUT.

Figure 2 shows these two steps. One thing to note is that the first clock cycle is just a reset; it assigns values to all the signals so they are known. Thus, for this figure, and all future figures, the cycle begins in the second clock cycle. The important thing to note in this figure is that the PC is being assigned  $PC + 4$  after executing the IF stage and IR has been assigned an instruction in that stage. In the next stage, register A and register B are assigned values that were read from the register file. The final clock cycle is bogus as the state machine was not updated.

## 2.2 LW/SW Instructions

LW and SW are the only two instructions allowed to access memory. They both have one step in common, and that is the memory address computation stage. In this step,

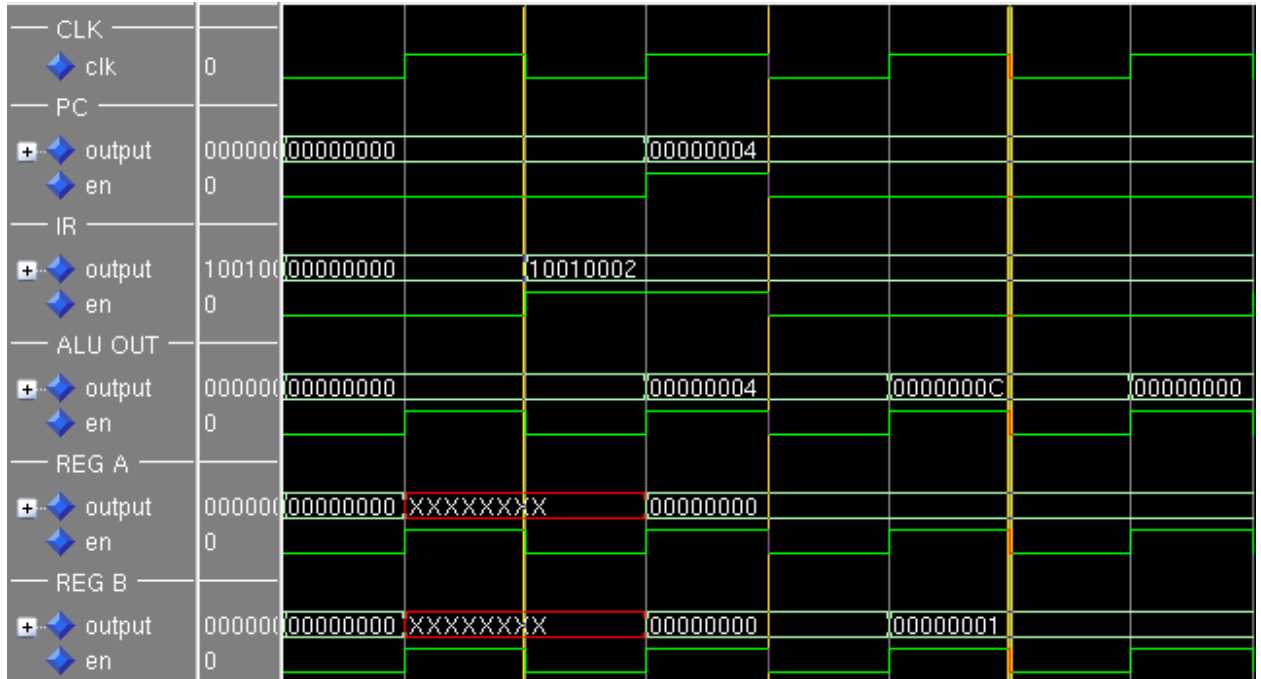


Figure 2: IF and ID stages. Both the first and last clock cycle have no meaning. The middle two are the one of interest.

ALUSrcA will be set to use register A. ALUSrcB will be set to use the bottom 16 bits of the instruction sign extended to 32 bits. These will be added by the ALU and used for the memory access.

Next is the memory access. The previously computed address is used here. Thus, in both the cases of LW and SW IorD is set to use the ALU OUT register. For LW, MemRead is asserted, and for SW, MemWrite is asserted.

At this point, SW is complete, but LW still has to write back. Thus, RegWrite is asserted, MemToReg is set to use the value stored in MDR, and RegDst is set to use RT.

Figure 3 shows the operation of LW. The first clock cycle is a reset. The second shows the IF stage. The third shows the ID stage. The fourth is where the memory address computation is occurring. Here,  $0x00FF$  is being added to  $R0$  as specified by the instruction. The ALU outputs  $FF$  as expected. Next, is the memory access... nothing happens here since the value of memory is kept constant for simplicity. Next, in the final clock cycle, the write back occurs, and  $R1$  gets the value of the memory.

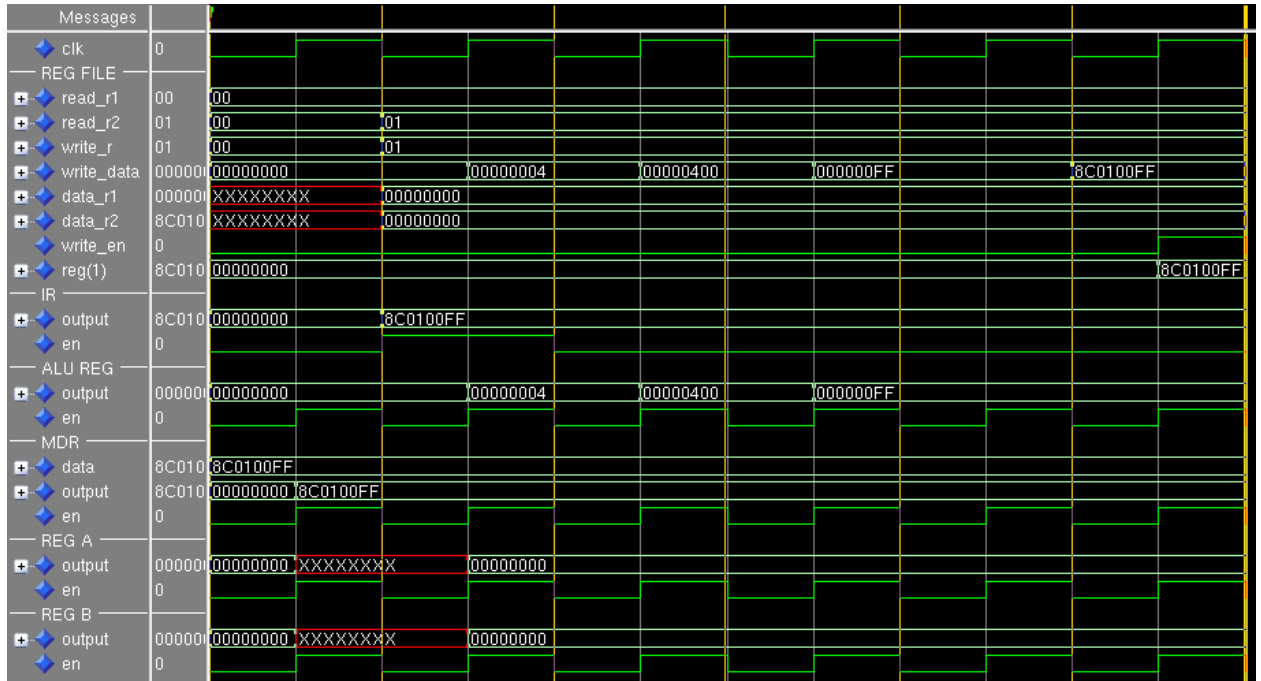


Figure 3: Shows the execution of a LW instruction

Similarly, Figure 4 shows the operation of SW. The first 4 cycles behave the same way. The final cycle is different in that it asserts a MemWrite signal and writes the data to memory.

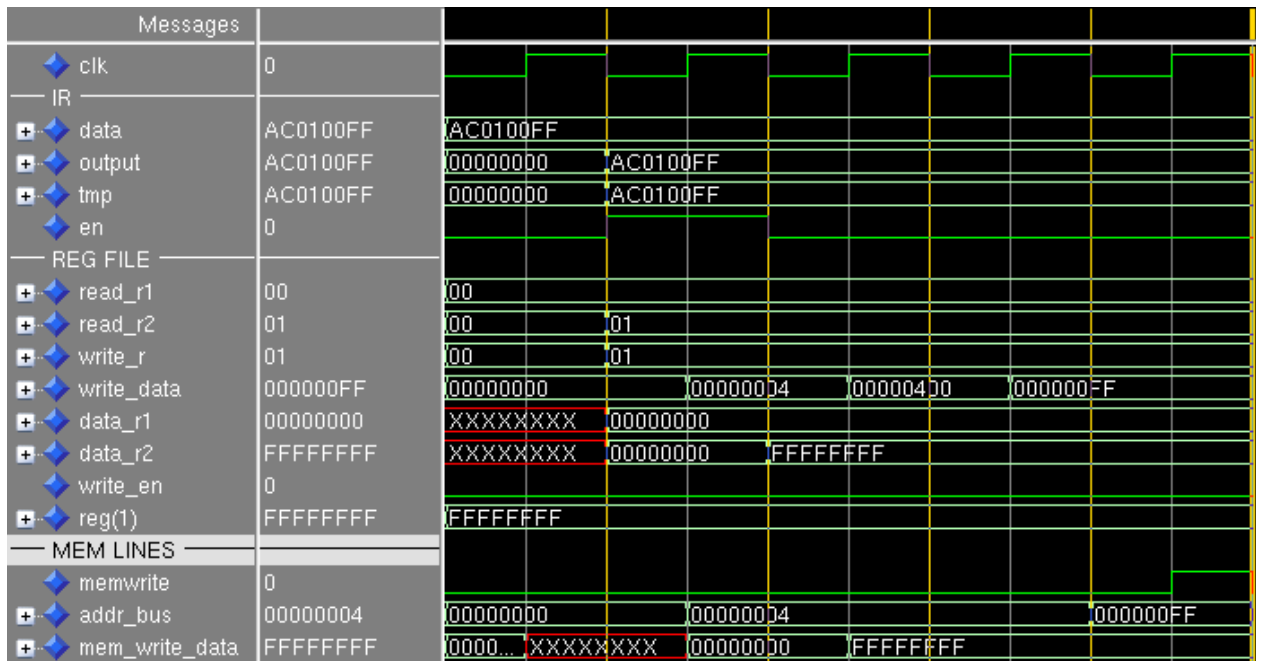


Figure 4: Shows the execution of a SW instruction

## 2.3 R Type Instructions

This section shows the correct functionality of the R Type instructions. Only add and sll are described in detail. The waveforms for the remaining are at the end of the section.

No further description is needed as only changing the ALU operation for the R Type instructions is done.

In general, R Type instructions consist of first performing the ALU operation specified, and writing that value back to the registers. For example, Figure 5 shows the waveform for an add instruction. First there is the reset cycle, then IF, and ID. Next is the execution stage. Here, the ALU takes the values read from the register file and performs an add on them. And the end of this cycle, write\_data has the value of  $R0 + R1$ . In the next cycle, the write back cycle,  $R2 \leq R0 + R1$  as expected.

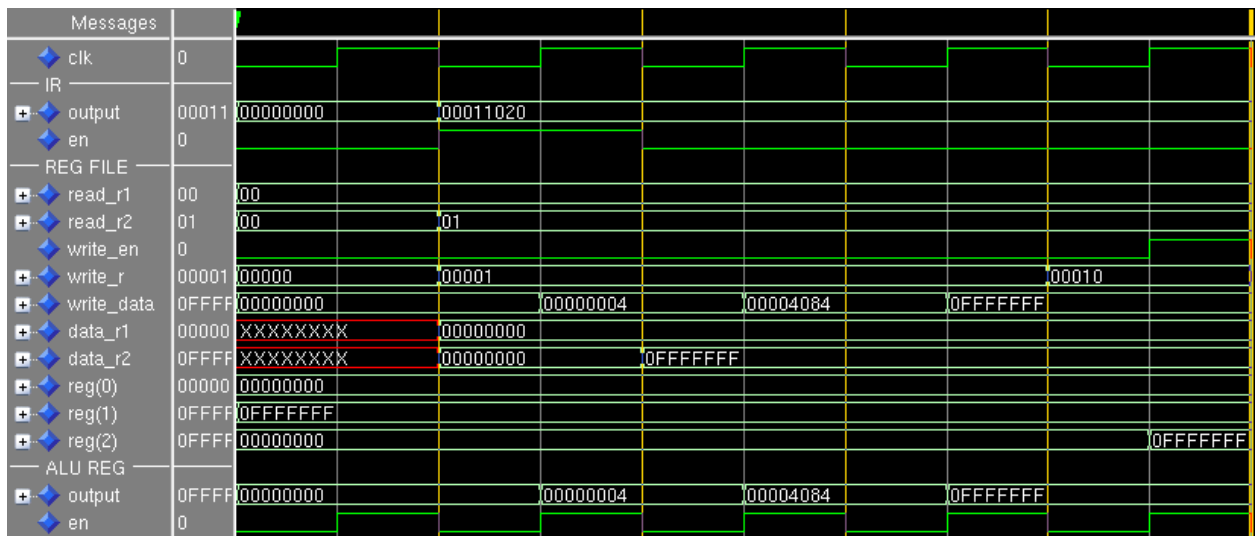


Figure 5: Shows the execution of a add instruction

The SLL is similar, except instead of adding 2 operands, it takes the B operand to the ALU and shifts it by an amount specified in the instruction. This is shown in Figure ???. The first clock cycle is the reset, followed by the IF, followed by ID, followed by the execution. In the execution, ALUSrcA is irrelevant. Operand B(R1) is '1', which will be left shifted by the amount of 2. Thus, the expected value is 4, and that is the value that is written back in the final clock cycle.

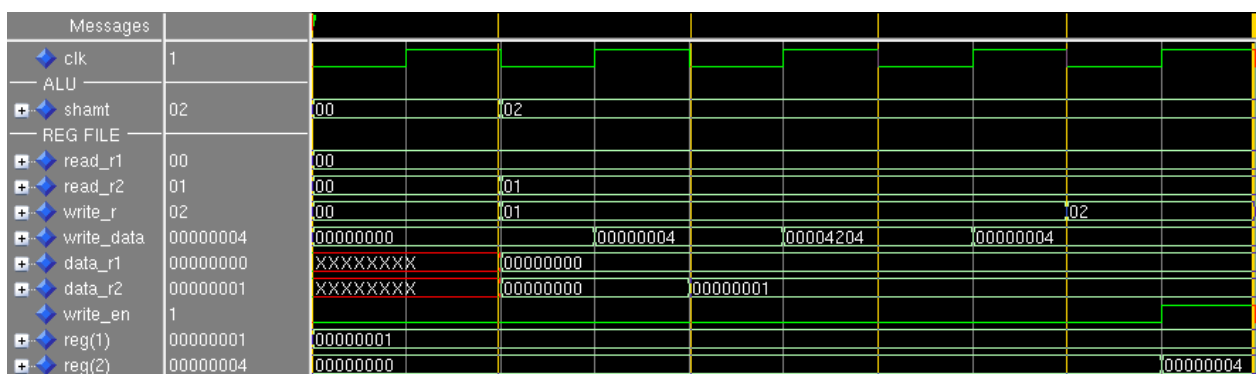


Figure 6: Shows the execution of a SLL instruction

The following are the figures for SUB, AND, OR, and SLT. Whats important to look at in these instructions are the operands and the final write back values. With that, it can be seen that each functions correctly.

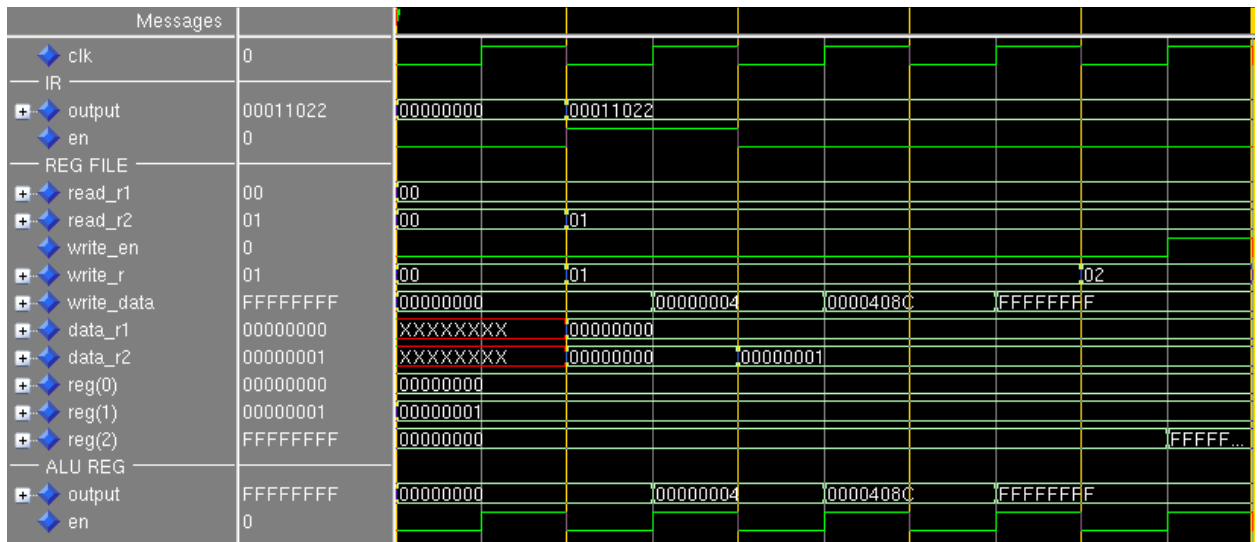


Figure 7: Shows the execution of a SUB instruction

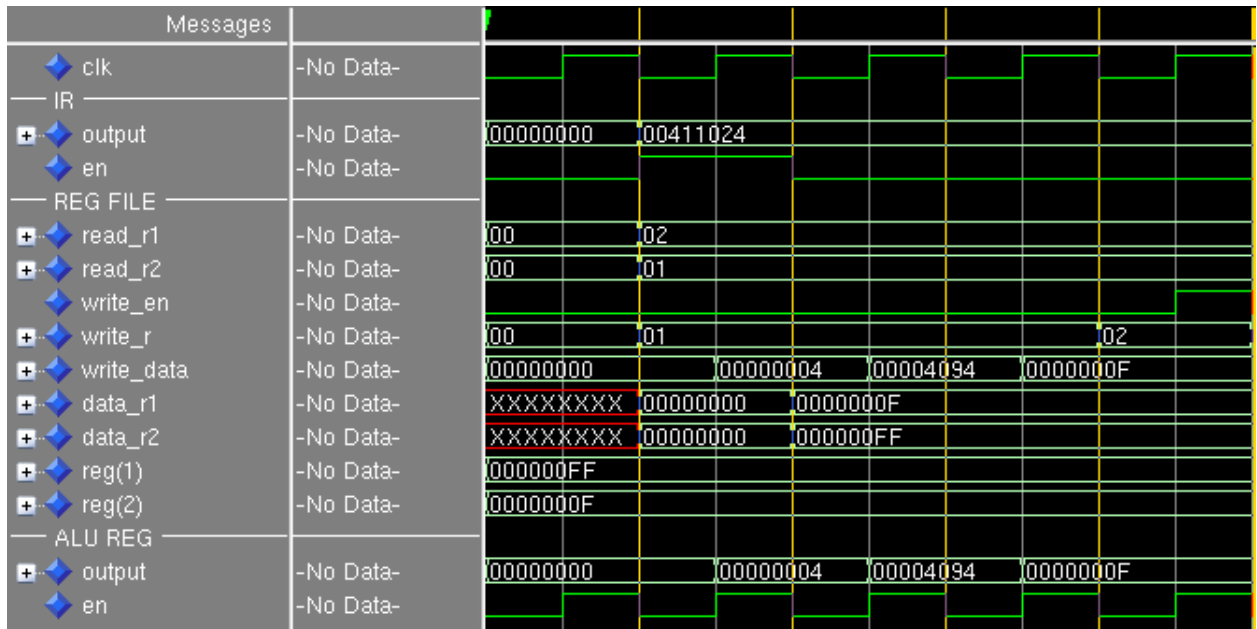


Figure 8: Shows the execution of a AND instruction



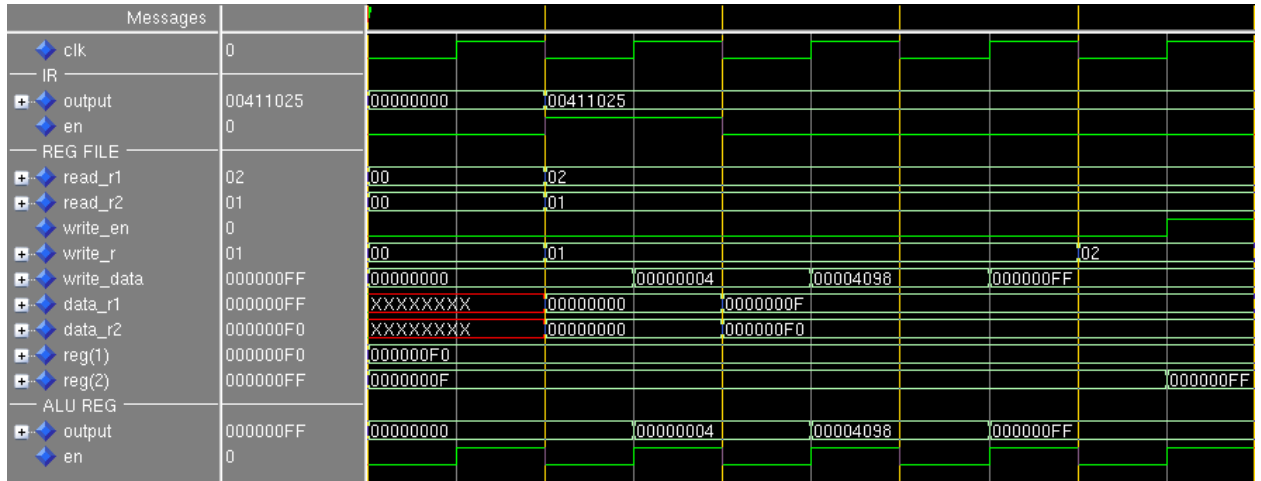


Figure 9: Shows the execution of a OR instruction


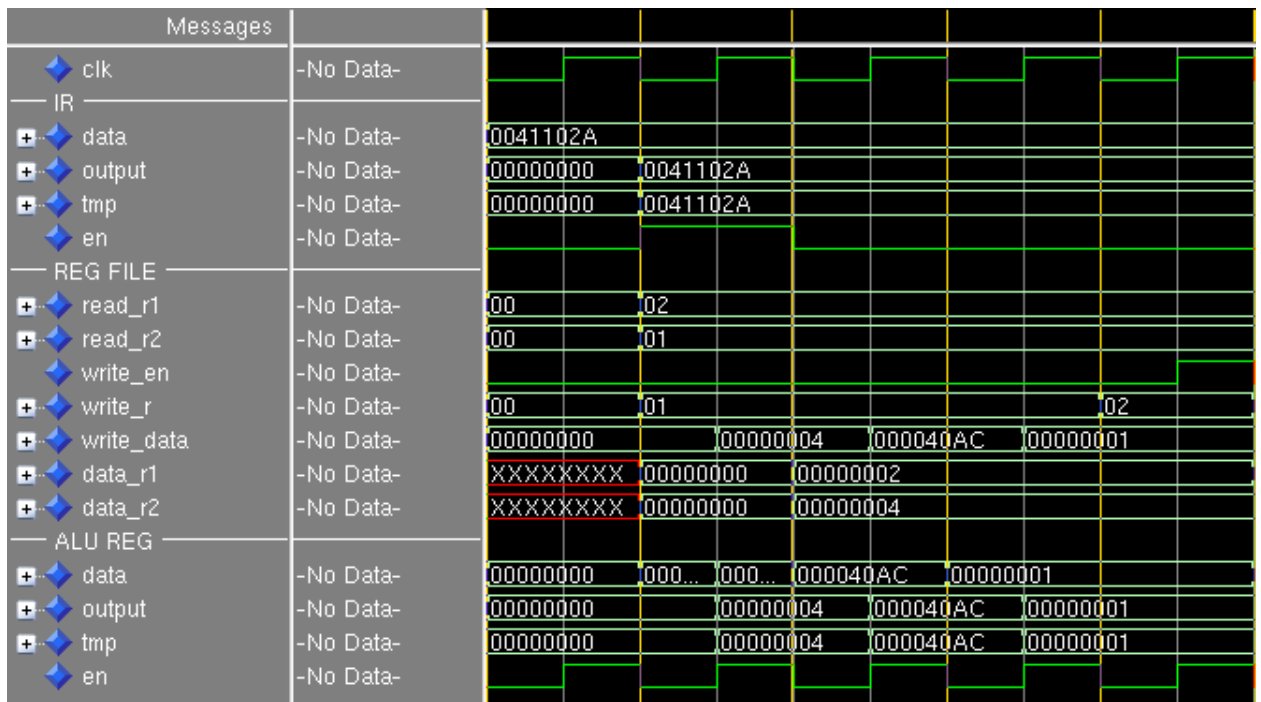


Figure 10: Shows the execution of a SLT instruction
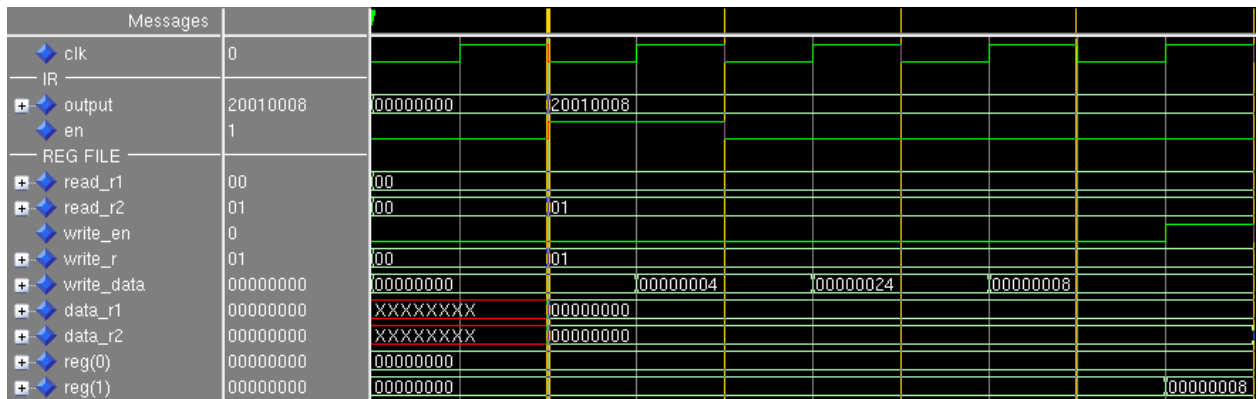
## 2.4 Immediate Instruction

Only one immediate instruction required testing, and the was ADDI. Its very similar to ADD, except that ALUSrcB is set to use the sign extended lower 16 bits of the instruction. Its waveform is shown in Figure 11. The first cycle is reset, the second is instruction fetch, third is instruction decode, fourth is execution. The lower 16 bits of this instruction are 8, which is being added to  $R0$ . The final clock cycle shows that 8 is written back as expected.



## 2.5 Branch and Jump

This section shows the correct functionality of BNE and JAL. BEQ and JMP are shown at the end of this section for completeness, however they are not annotated as the instructions are very similar to BNE and JAL.

The correct functionality for BNE is shown in Figure 12. For branch instructions, the target address is available after the ID stage. Thus, as soon as the appropriate signals have propagated from the ALU, we can branch. For BNE, the control unit will set ALUSrcA to register A. ALUSrcB will be set to allow register B. These two will be compared in the ALU during the execution stage. Along with those signals, BNE needs to assert the PCWriteCondNEq signal to indicate a branch when not equal. The branch occurs in the execution stage, as that is when PC is written with its new value. In Figure 12, the lower 16 bits are 2. Sign extended and shifted left by two makes 8. Thus,  $PC + 4 + 8 = C$ , as the original PC started off at 0. This is the value that is written to the PC as can be seen.

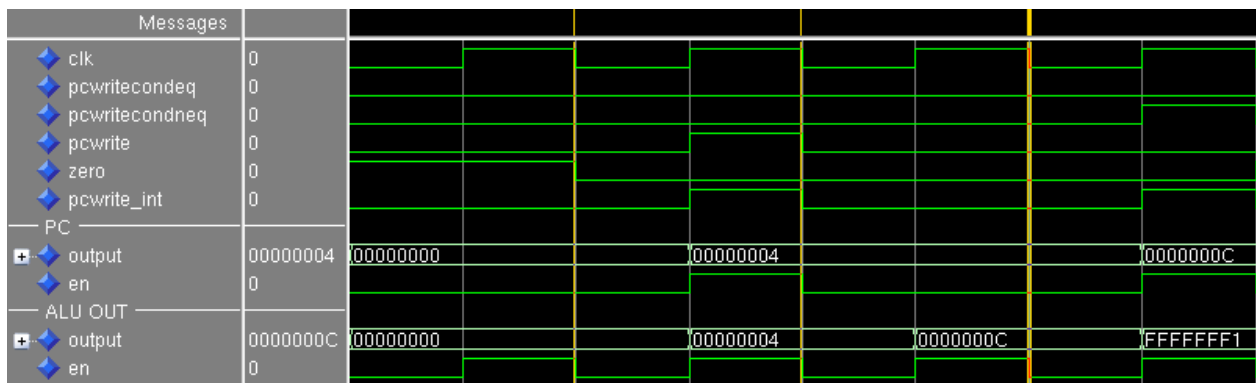


Figure 12: Shows the execution of a BNE instruction.

Jumping is similar to a branch, however it uses instruction[26-0] shifted left by 2 for the lower 28 bits. The higher bits are determined by PC[31-28]. JAL, shown in Figure 13, does more than just jump. It also writes the value of the PC to *R31*. The instruction in Figure 13 stores the value of PC as expected into *R31* in the final clock cycle. The lower 26 bits of the instruction are 8, thus 0x20 is the expected jump value, the same value that PC gets in the final clock cycle.

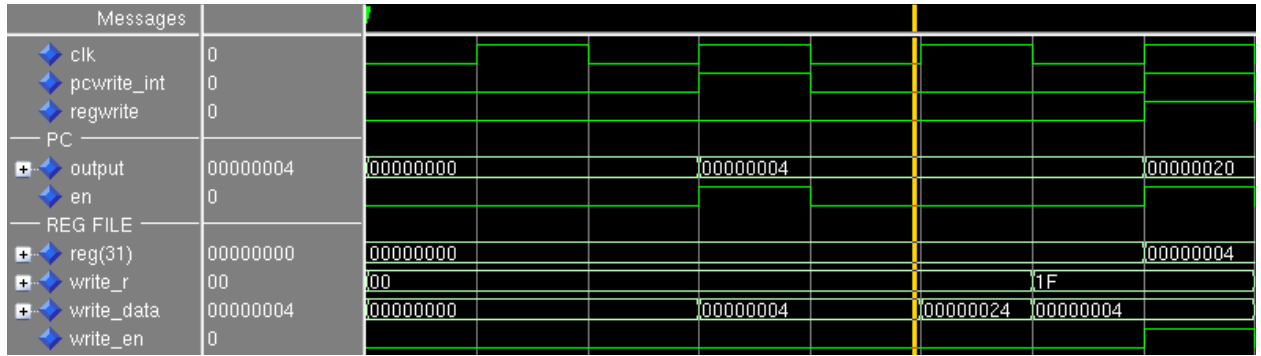


Figure 13: Shows the execution of a JAL instruction

The following figures(13 and 15 show similar instructions J and BEQ.

 


Figure 14: Shows the execution of a J instruction

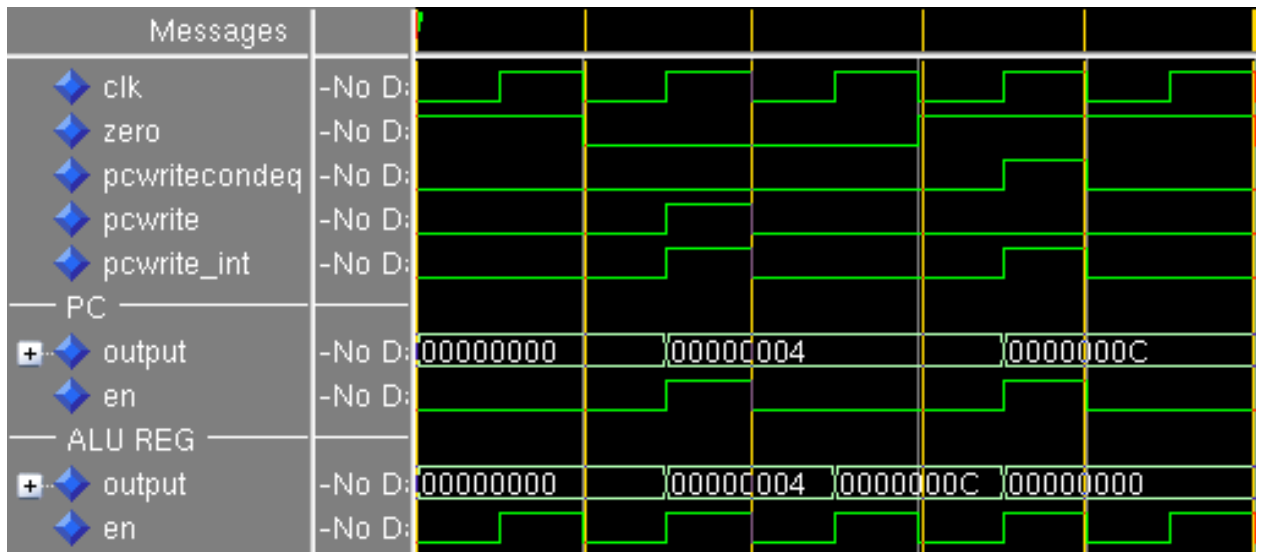


Figure 15: Shows the execution of a BEQ instruction

## 2.6 LUI

Since the ALU already has the capability to do shift operations on ALU port B operands, nothing needs to be added to the datapath. This instruction can be executed by 3 instructions already described. The instructions needed are SLL, which is done by 16 bits. Next, we can use an AND the lower upper 16 bits of the register we want to LUI into with 1's. This clears out the top bits. This leaves one final OR with the result of SLL and the register we want to LUI into.

## 2.7 Exception Handling

Exception handling requires two additional registers and addition control signals. The registers needed are the cause register and the EPC. This datapath must allow for two different types of exceptions. First, the arithmetic overflow exception. This can only occur during the execution stage, and may not be caused by the control unit. The second is undefined instruction. Here, there are two possibilities. First, there can be an unknown opcode. Second, there can be an unknown function for an R-Type. The design here is to let the ALU assert arithmetic overflow exceptions, and the control unit will assert the unknown operation exception. When these are asserted, there will be a jump to some hard-wired memory address, in this case 0x4 for simplicity.

## 3 Unfinished

1. ALU does not generate overflow
2. There is no testbench for exception handling

Other than that, and a bug with the IR that does not produce any bad results, everything works.

## A Code

```
1  -----
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : mips_lib.vhdl
5  — Creation Date : 06/11/2009
6  — Description :
7  —
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13
14 package mips_lib is
15     constant DATA_WIDTH : integer           := 32;
16     constant ADDR_WIDTH  : integer           := 32;
17
18     constant rOpcode      : bit_vector(5 downto 0) := "000000";
19     constant jOpcode      : bit_vector(5 downto 0) := "000010";
20     constant jalOpcode    : bit_vector(5 downto 0) := "000011";
21     constant addiOpcode   : bit_vector(5 downto 0) := "001000";
22     constant andiOpcode   : bit_vector(5 downto 0) := "001100";
23     constant beqOpcode    : bit_vector(5 downto 0) := "000100";
24     constant bneOpcode    : bit_vector(5 downto 0) := "000101";
25     constant lwOpcode     : bit_vector(5 downto 0) := "100011";
26     constant swOpcode     : bit_vector(5 downto 0) := "101011";
27
28     constant addFunc      : bit_vector(5 downto 0) := "100000";
29     constant subFunc      : bit_vector(5 downto 0) := "100010";
30     constant andFunc      : bit_vector(5 downto 0) := "100100";
```

```

31    constant orFunc      : bit_vector(5 downto 0) := "100101";
32    constant sltFunc     : bit_vector(5 downto 0) := "101010";
33    constant sllFunc     : bit_vector(5 downto 0) := "000000";
34
35    constant UDEXP       : std_logic_vector(31 downto 0) := x"00000003";
36    constant OVFXP      : std_logic_vector(31 downto 0) := x"00000001";
37
38
39
40    type t_aluSrcA       is (ASA_PC, ASA_REG_A);
41    type t_aluSrcB       is (ASB_REGB, ASB_FOUR, ASB_SEXT, ASB_SEXTS);
42    type t_aluOp         is (AOP_AND, AOP_OR, AOP_ADD, AOP_SUB, AOP_SLT,
        AOP_NOR, AOP_SLL);
43    type t_pcSrc         is (PS_PCINC, PS_ALUOUT, PS_JMP, PS_FOUR);
44    type t_regDst        is (RD_RT, RD_RD, RD_RA);
45    type t_iord          is (IOD_PC, IOD_ALUOUT);
46    type t_memToReg      is (MTR_ALUOUT, MTR_MDR, MTR_PC);
47    type t_comp          is (eq, ne, gt, lt, lte, gte);
48    type t_microinstr is (
49        s_if,      — Instruction Fetch
50        s_id       — Instruction Decode
51    );
52
53
54 end package;

```

Listing 1: mips\_lib.vhdl

```

1  -----
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : reg.vhdl
5  — Creation Date  : 06/11/2009
6  — Description:
7  —
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13
14 -----
15 Entity reg is
16 -----
17 generic
18 (
19     SIZE  : natural := 32;
20     DELAY : time := 0 ns
21 );
22
23
24 port
25 (
26     en      : in std_logic;
27     data    : in std_logic_vector((SIZE-1) downto 0);
28     output  : out std_logic_vector((SIZE-1) downto 0)
29 );
30 end entity;
31

```

```

32
33
34 Architecture reg_1 of reg is
35
36     signal tmp : std_logic_vector((SIZE-1) downto 0) := (others => '0');
37 begin
38     process(en)
39     begin
40         if(en='1') then
41             tmp <= data;
42         end if;
43     end process;
44     output <= tmp;
45 end architecture reg_1;

```

Listing 2: Register

```

1
2 — Author(s) : Jay Mundrawala <mundra@ir.iit.edu>
3 —
4 — File : reg_file.vhdl
5 — Creation Date : 06/11/2009
6 — Description:
7 —
8
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use ieee.std_logic_arith.all;
14 use ieee.std_logic_unsigned.all;
15
16 Entity reg_file is
17
18 generic
19 (
20     SIZE : natural :=32;
21     DELAY : time := 0 ns
22 );
23 port
24 (
25     clk : in std_logic;
26     write_en : in std_logic;
27     read_r1 : in std_logic_vector(4 downto 0);
28     read_r2 : in std_logic_vector(4 downto 0);
29     write_r : in std_logic_vector(4 downto 0);
30     write_data : in std_logic_vector((SIZE-1) downto 0);
31     data_r1 : out std_logic_vector((SIZE-1) downto 0);
32     data_r2 : out std_logic_vector((SIZE-1) downto 0)
33 );
34 end entity;
35
36
37
38 Architecture reg_file_1 of reg_file is
39
40     type t_reg is array (0 to 31) of std_logic_vector(31 downto 0);
41     signal reg : t_reg := ((others => (others=>'0')));
42

```

```

43 begin
44     process( clk )
45     begin
46         if( clk 'event and clk='0') then
47             data_r1 <= reg( CONV_INTEGER( read_r1 )) after DELAY/2;
48             data_r2 <= reg( CONV_INTEGER( read_r2 )) after DELAY/2;
49         elsif( clk 'event and clk='1') then
50             if( write_en ='1') then
51                 reg( CONV_INTEGER( write_r )) <= write_data after DELAY;
52             end if;
53         end if;
54         reg(0) <= ( others => '0' );
55     end process;
56 end architecture reg_file_1;

```

Listing 3: Register File

```

1  -----
2  -- Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  --
4  -- File           : alu.vhdl
5  -- Creation Date  : 21/11/2009
6  -- Description:
7  --
8  -----
9
10 library IEEE;
11 use work.mips_lib.all;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.numeric_std.all;
14 -----
15 Entity alu is
16 -----
17 port
18 (
19     op_A      : in std_logic_vector(31 downto 0);
20     op_B      : in std_logic_vector(31 downto 0);
21     shamt     : in std_logic_vector(4  downto 0);
22     alu_ctrl  : in t_aluOp;
23     f         : out std_logic_vector(31 downto 0);
24     zero      : out std_logic;
25     overflow  : out std_logic
26 );
27 end entity;
28
29
30
31 -----
32 Architecture alu_1 of alu is
33 -----
34 -- from http://www.csee.umbc.edu/~squire/download/bshift.vhdl
35 function to_integer(sig : std_logic_vector) return integer is
36     variable num : integer := 0; -- descending sig as integer
37 begin
38     for i in sig'range loop
39         if sig(i)='1' then
40             num := num*2+1;
41         else
42             num := num*2;

```

```

43     end if;
44     end loop; -- i
45     return num;
46 end function to_integer;
47 CONSTANT DELAY : time := 0 ns;
48 signal value    : std_logic_vector(31 downto 0);
49 begin
50     process(alu_ctrl, op_A, op_B)
51     begin
52         case alu_ctrl is
53             when AOP_AND =>
54                 value <= op_A and op_B after DELAY;
55             when AOP_OR =>
56                 value <= op_A or op_B after DELAY;
57             when AOP_ADD =>
58                 value <= std_logic_vector(signed(op_A) + signed(op_B))
59                     after DELAY;
60             when AOP_SUB =>
61                 value <= std_logic_vector(signed(op_A) - signed(op_B))
62                     after DELAY;
63             when AOP_SLT =>
64                 if(signed(op_A) < signed(op_B)) then
65                     value <= (others => '0');
66                     value(0) <= '1';
67                 else
68                     value <= (others => '0');
69                 end if;
70             when AOP_NOR =>
71                 value <= NOT (op_A or op_B) after DELAY;
72             when AOP_SLL =>
73                 value <= to_stdlogicvector(to_bitvector(op_B) sll
74                     to_integer(shamt));
75             when others =>
76                 value <= (others => '1');
77         end case;
78     end process;
79     f <= value;
80     zero <= '1' when value = x"00000000" else
81         '0';
82 end architecture alu_1;

```

Listing 4: ALU

---

```

1  --
2  -- Author(s)    : Jay Mundrawala <mundra@ir.iit.edu>
3  --
4  -- File         : datapath.vhdl
5  -- Creation Date : 06/11/2009
6  -- Description:
7  --
8  --
9  --
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips.lib.all;
14
15 --
16 Entity datapath is

```

---



---

```

17
18     port(
19         clk                : in std_logic;
20     — Control Unit
21         PCWriteCondEq      : in std_logic;
22         PCWriteCondNEq     : in std_logic;
23         PCWrite             : in std_logic;
24         IorD                : in t_iord;
25         MemRead             : in std_logic;
26         MemWrite            : in std_logic;
27         MemToReg            : in t_memToReg;
28         IRWrite             : in std_logic;
29         RegWrite            : in std_logic;
30         RegDst              : in t_regDst;
31         ALUSrcA             : in t_aluSrcA;
32         ALUSrcB             : in t_aluSrcB;
33         PCSource            : in t_pcSrc;
34         ALUOp               : in t_aluOp;
35         UndefInstrEx        : in std_logic;
36         OverflowEx          : out std_logic;
37         Exception           : in std_logic;
38
39     — Memory
40         mem_data_out        : in std_logic_vector((DATA_WIDTH-1) downto 0);
41         mem_read            : out std_logic;
42         addr_bus            : out std_logic_vector((DATA_WIDTH-1) downto 0);
43         mem_write_data      : out std_logic_vector((DATA_WIDTH-1) downto 0);
44     );
45
46 end entity;
47
48
49
50


---


51 Architecture datapath_1 of datapath is
52


---


53     component reg
54     generic (
55         SIZE : natural := 32;
56         DELAY : time := 0 ns
57     );
58     port (
59         en      : in std_logic;
60         data    : in std_logic_vector((SIZE-1) downto 0);
61         output   : out std_logic_vector((SIZE-1) downto 0)
62     );
63 end component reg;
64
65     component reg_file
66     generic (
67         SIZE : natural := 32;
68         DELAY : time := 0 ns
69     );
70     port (
71         clk      : in std_logic;
72         write_en  : in std_logic;
73         read_r1   : in std_logic_vector(4 downto 0);
74         read_r2   : in std_logic_vector(4 downto 0);

```

```

75         write_r      : in std_logic_vector(4 downto 0);
76         write_data    : in std_logic_vector((SIZE-1) downto 0);
77         data_r1       : out std_logic_vector((SIZE-1) downto 0);
78         data_r2       : out std_logic_vector((SIZE-1) downto 0)
79     );
80 end component reg_file;
81
82 component alu
83     port(
84         op_A      : in std_logic_vector(31 downto 0);
85         op_B      : in std_logic_vector(31 downto 0);
86         shamt     : in std_logic_vector(4 downto 0);
87         alu_ctrl  : in t_aluOp;
88         f         : out std_logic_vector(31 downto 0);
89         zero      : out std_logic;
90         overflow  : out std_logic
91     );
92 end component alu;
93
94 signal PCDATA_int      : std_logic_vector((DATA_WIDTH - 1) downto 0);
95 signal PCOUT_int       : std_logic_vector((DATA_WIDTH - 1) downto 0);
96 signal instruction     : std_logic_vector((DATA_WIDTH - 1) downto 0);
97 signal mdreg           : std_logic_vector((DATA_WIDTH - 1) downto 0);
98 signal rf_write_data   : std_logic_vector((DATA_WIDTH - 1) downto 0);
99 signal rf_write_reg    : std_logic_vector(4 downto 0);
100 signal alu_a           : std_logic_vector((DATA_WIDTH - 1) downto 0);
101 signal alu_b           : std_logic_vector((DATA_WIDTH - 1) downto 0);
102 signal alu_reg_in      : std_logic_vector((DATA_WIDTH - 1) downto 0);
103 signal alu_reg_out     : std_logic_vector((DATA_WIDTH - 1) downto 0);
104 signal rega_in         : std_logic_vector((DATA_WIDTH - 1) downto 0);
105 signal regb_in         : std_logic_vector((DATA_WIDTH - 1) downto 0);
106 signal rega_out        : std_logic_vector((DATA_WIDTH - 1) downto 0);
107 signal regb_out        : std_logic_vector((DATA_WIDTH - 1) downto 0);
108 signal epc_out         : std_logic_vector((DATA_WIDTH - 1) downto 0);
109 signal cause_out       : std_logic_vector((DATA_WIDTH - 1) downto 0);
110 signal cause_data      : std_logic_vector((DATA_WIDTH - 1) downto 0);
111 signal instr_sext      : std_logic_vector((DATA_WIDTH - 1) downto 0);
112 signal instr_sexths    : std_logic_vector((DATA_WIDTH - 1) downto 0);
113 signal zero            : std_logic;
114 signal overflow        : std_logic;
115 signal do_cause        : std_logic;
116 signal PCWrite_int     : std_logic;
117 begin
118     OverflowEx <= overflow;
119     RF: reg_file
120     port map(
121         clk => clk ,
122         write_en => RegWrite ,
123         read_r1 => instruction(25 downto 21) ,
124         read_r2 => instruction(20 downto 16) ,
125         write_r => rf_write_reg ,
126         write_data => rf_write_data ,
127         data_r1 => rega_in ,
128         data_r2 => regb_in
129     );
130
131     PC: reg
132     port map(

```

```

133         en      => PCWRITE_int ,
134         data     => PCDATA_int ,
135         output   => PCOUT_int
136     );
137
138     IR: reg
139     port map(
140         en      => IRWrite ,
141         data     => mem_data_out ,
142         output   => instruction
143     );
144     AOR: reg
145     port map(
146         en => clk ,
147         data => alu_reg_in ,
148         output => alu_reg_out
149     );
150
151     MDR: reg
152     port map(
153         en      => clk ,
154         data     => mem_data_out ,
155         output   => mdreg
156     );
157
158     RRA: reg
159     port map(
160         en      => clk ,
161         data     => rega_in ,
162         output   => rega_out
163     );
164
165     RRB: reg
166     port map(
167         en      => clk ,
168         data     => regb_in ,
169         output   => regb_out
170     );
171
172     ALUU: alu
173     port map(
174         op_A      => alu_a ,
175         op_B      => alu_b ,
176         alu_ctrl  => ALUOp,
177         f         => alu_reg_in ,
178         zero      => zero ,
179         shamt     => instruction(10 downto 6) ,
180         overflow  => overflow
181     );
182
183     EPC: reg
184     port map(
185         en      => Exception ,
186         data     => PCOUT_int ,
187         output   => epc_out
188     );
189
190     do_cause <= UndefInstrEx or overflow;

```

```

191 CAUSE: reg
192 port map(
193         en      => do_cause ,
194         data    => cause_data ,
195         output => cause_out
196     );
197
198 mem_write_data <= regb_out;
199
200 CAUSEPROC: process(do_cause)
201 begin
202     if(do_cause='1') then
203         if(UndefInstrEx = '1') then
204             cause_data <= UDEXP;
205         else
206             cause_data <= OVFXP;
207         end if;
208     end if;
209 end process;
210 ——— PC Write/Branch MUX ———
211 PCFinal : process(PCWriteCondEq, PCWriteCondNEq, PCWrite)
212 begin
213     if((PCWriteCondEq='1' and zero='1') or (PCWriteCondNEq='1' and zero
214         = '0') or PCWrite='1') then
215         PCWRITE_int <= '1';
216     else
217         PCWRITE_int <= '0';
218     end if;
219 end process;
220 — PCSource Mux —
221 PCSMux: process(PCSource, alu_reg_out, alu_reg_in)
222 begin
223     if(PCSource = PS_PCINC) then
224         PCDATA_int <= alu_reg_in;
225     elsif(PCSource = PS_ALUOUT) then
226         PCDATA_int <= alu_reg_out;
227     elsif(PCSource = PS_JMP) then
228         PCDATA_int <= PCOUT_int(31 downto 28) & instruction(25 downto
229             0) & "00";
230     elsif(PCSource = PS_FOUR) then
231         PCDATA_int <= x"00000004";
232     end if;
233 end process;
234 — IorD Mux
235 IorDMux : process (PCOUT_int, alu_reg_out, IorD)
236 begin
237     if(IorD = IOD_PC) then
238         addr_bus <= PCOUT_int;
239     else
240         addr_bus <= alu_reg_out;
241     end if;
242 end process;
243
244 — MemToReg Mux —
245 MTRMux: process (MemToReg, mdreg, alu_reg_out)
246 begin

```

```

247         if(MemToReg = MTR.ALUOUT) then
248             rf_write_data <= alu_reg_out;
249         elsif(MemToReg = MTR.MDR) then
250             rf_write_data <= mdreg;
251         else
252             rf_write_data <= PCOUT_int;
253         end if;
254     end process;
255
256     — RegDst Mux —
257     RDMux : process (instruction , RegDst)
258     begin
259         if(RegDst = RD_RT) then
260             rf_write_reg <= instruction(20 downto 16);
261         elsif(RegDst = RD_RD) then
262             rf_write_reg <= instruction(15 downto 11);
263         else
264             rf_write_reg <= "11111";
265         end if;
266     end process;
267
268     — ALUSrcA Mux —
269     ALUSA: process (ALUSrcA, PCOUT_int, rega_out)
270     begin
271         if(ALUSrcA = ASA_PC) then
272             alu_a <= PCOUT_int;
273         else
274             alu_a <= rega_out;
275         end if;
276     end process;
277
278     — ALUSrcB Mux —
279     ALUSB: process (ALUSrcB, regb_out, instr_sext, instr_sexts)
280     begin
281         if(ALUSrcB = ASB_REGB) then
282             alu_b <= regb_out;
283         elsif(ALUSrcB = ASB_FOUR) then
284             alu_b <= "0000000000000000000000000000100";
285         elsif(ALUSrcB = ASB_SEXT) then
286             alu_b <= instr_sext;
287         else
288             alu_b <= instr_sexts;
289         end if;
290     end process;
291
292     — Sign Extend and Shift —
293     SEXTS: process(instruction)
294     begin
295         instr_sext <= (31 downto 16 => instruction(15)) & instruction(15
            downto 0);
296         instr_sexts <= (31 downto 18 => instruction(15)) & instruction(15
            downto 0) & "00";
297     end process;
298
299 end architecture datapath_1;

```

Listing 5: Datapath

```

2  -- Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  --
4  -- File           : ADDI_Testbench.vhdl
5  -- Creation Date  : 21/11/2009
6  -- Description:
7  --
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 -----
16 Entity ADDI_Testbench is
17 -----
18 end entity;
19
20
21 -----
22 Architecture ADDI_Testbench_1 of ADDI_Testbench is
23 -----
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27         port(
28             clk           : in std_logic;
29             -- Control Unit
30             PCWriteCondEq : in std_logic;
31             PCWriteCondNEq : in std_logic;
32             PCWrite       : in std_logic;
33             IorD          : in t_iord;
34             MemRead       : in std_logic;
35             MemWrite      : in std_logic;
36             MemToReg      : in t_memToReg;
37             IRWrite       : in std_logic;
38             RegWrite      : in std_logic;
39             RegDst        : in t_regDst;
40             ALUSrcA       : in t_aluSrcA;
41             ALUSrcB       : in t_aluSrcB;
42             PCSource      : in t_pcSrc;
43             ALUOp         : in t_aluOp;
44
45             UndefInstrEx  : in std_logic;
46             OverflowEx    : out std_logic;
47             Exception     : in std_logic;
48
49             --Memory
50             mem_data_out  : in  std_logic_vector((DATA_WIDTH-1) downto 0);
51             mem_read      : out std_logic;
52             addr_bus      : out std_logic_vector((DATA_WIDTH-1) downto 0);
53             mem_write_data : out std_logic_vector((DATA_WIDTH-1) downto 0)
54         );
55     end component datapath;
56
57     signal PCWriteCondEq : std_logic;
58     signal PCWriteCondNEq : std_logic;
59     signal PCWrite       : std_logic;

```

```

60     signal IorD           : t_iord;
61     signal MemRead        : std_logic;
62     signal MemWrite       : std_logic;
63     signal MemToReg       : t_memToReg;
64     signal IRWrite        : std_logic;
65     signal RegWrite       : std_logic;
66     signal RegDst         : t_regDst;
67     signal ALUSrcA        : t_aluSrcA;
68     signal ALUSrcB        : t_aluSrcB;
69     signal PCSource       : t_pcSrc;
70     signal ALUOp          : t_aluOp;
71
72     signal UndefInstrEx   : std_logic;
73     signal OverflowEx     : std_logic;
74     signal Exception      : std_logic;
75
76     —Memory
77     signal mem_data_out   : std_logic_vector((DATA_WIDTH-1) downto 0);
78     signal mem_read       : std_logic;
79     signal addr_bus       : std_logic_vector((DATA_WIDTH-1) downto 0);
80     signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
81
82 begin
83     —Create a clock.
84     PROCESS
85     BEGIN
86         Clk <= '0';
87         WAIT FOR T/2;
88         Clk <= '1';
89         WAIT FOR T/2;
90     END PROCESS;
91
92     DUT: entity work.datapath
93     port map(
94         clk           => clk ,
95         PCWriteCondEq => PCWriteCondEq ,
96         PCWriteCondNEq => PCWriteCondNEq ,
97         PCWrite       => PCWrite ,
98         IorD          => IorD ,
99         MemRead       => MemRead ,
100        MemWrite      => MemWrite ,
101        MemToReg      => MemToReg ,
102        IRWrite       => IRWrite ,
103        RegWrite      => RegWrite ,
104        RegDst        => RegDst ,
105        ALUSrcA       => ALUSrcA ,
106        ALUSrcB       => ALUSrcB ,
107        PCSource      => PCSource ,
108        ALUOp         => ALUOp ,
109        UndefInstrEx  => UndefInstrEx ,
110        OverflowEx    => OverflowEx ,
111        Exception     => Exception ,
112
113        mem_data_out  => mem_data_out ,
114        mem_read      => mem_read ,
115        addr_bus      => addr_bus ,
116        mem_write_data => mem_write_data
117    );

```

```

118
119 PROCESS
120 BEGIN
121     PCWriteCondEq <= '0';
122     PCWrite <= '0';
123     IorD <= IOD_PC;
124     MemRead <= '0';
125     MemWrite <= '0';
126     MemToReg <= MTR_ALUOUT;
127     IRWrite <= '0';
128     RegWrite <= '0';
129     RegDst <= RD_RT;
130     ALUSrcA <= ASA_PC;
131     ALUSrcB <= ASB_REGB;
132     PCSrc <= PS_PCINC;
133     ALUOp <= AOP_AND;
134
135     —  $R[1] \leq R[0] + 8$ 
136     mem_data_out <= "001000" & "00000" & "00001" & "0000000000001000";
137     wait for T;
138
139     — IF
140     MemRead <= '1';
141     ALUSrcA <= ASA_PC;
142     IorD <= IOD_PC;
143     IRWrite <= '1';
144     ALUSrcB <= ASB_FOUR;
145     ALUOp <= AOP_ADD;
146     PCWrite <= '0';
147     PCSrc <= PS_PCINC;
148     wait for T/2;
149     PCWrite <= '1';
150     wait for T/2;
151
152     — ID/Bra Calc
153     PCWrite <= '0';
154     MemRead <= '0';
155     IRWrite <= '0';
156     ALUSrcA <= ASA_PC;
157     ALUSrcB <= ASB_SEXTS;
158     PCSrc <= PS_PCINC;
159     ALUOp <= AOP_ADD;
160     wait for T;
161
162     — Execute
163     ALUSrcA <= ASA_REG_A;
164     ALUSrcB <= ASB_SEXT;
165     ALUOp <= AOP_ADD;
166     wait for T;
167
168
169     — Write Back
170     MemToReg <= MTR_ALUOUT;
171     RegDst <= RD_RT;
172     wait for T/2;
173     RegWrite <= '1';
174     wait for T/2;
175

```



```

176
177     END PROCESS;
178
179 end architecture ADDI_Testbench_1;

```

Listing 6: ADDI\_Testbench

```

1  -----
2  -- Author(s)    : Jay Mundrawala <mundra@ir.iit.edu>
3  --
4  -- File         : ADD_Testbench.vhdl
5  -- Creation Date : 21/11/2009
6  -- Description :
7  --
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 -----
16 Entity ADD_Testbench is
17 -----
18 end entity;
19
20
21 -----
22 Architecture ADD_Testbench_1 of ADD_Testbench is
23 -----
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27         port(
28             clk                : in std_logic;
29             -- Control Unit
30             PCWriteCondEq      : in std_logic;
31             PCWriteCondNEq     : in std_logic;
32             PCWrite             : in std_logic;
33             IorD                : in t_iord;
34             MemRead             : in std_logic;
35             MemWrite            : in std_logic;
36             MemToReg            : in t_memToReg;
37             IRWrite             : in std_logic;
38             RegWrite            : in std_logic;
39             RegDst              : in t_regDst;
40             ALUSrcA             : in t_aluSrcA;
41             ALUSrcB             : in t_aluSrcB;
42             PCSource            : in t_pcSrc;
43             ALUOp               : in t_aluOp;
44
45             UndefInstrEx       : in std_logic;
46             OverflowEx         : out std_logic;
47             Exception           : in std_logic;
48
49             --Memory
50             mem_data_out        : in  std_logic_vector((DATA_WIDTH-1) downto 0);
51             mem_read             : out std_logic;
52             addr_bus             : out std_logic_vector((DATA_WIDTH-1) downto 0);

```

```

53         mem_write_data : out std_logic_vector((DATA_WIDTH-1) downto 0)
54     );
55 end component datapath;
56
57 signal PCWriteCondEq : std_logic;
58 signal PCWriteCondNEq : std_logic;
59 signal PCWrite       : std_logic;
60 signal IorD          : t_iord;
61 signal MemRead       : std_logic;
62 signal MemWrite      : std_logic;
63 signal MemToReg      : t_memToReg;
64 signal IRWrite       : std_logic;
65 signal RegWrite      : std_logic;
66 signal RegDst        : t_regDst;
67 signal ALUSrcA       : t_aluSrcA;
68 signal ALUSrcB       : t_aluSrcB;
69 signal PCSource      : t_pcSrc;
70 signal ALUOp         : t_aluOp;
71
72 signal UndefInstrEx   : std_logic;
73 signal OverflowEx    : std_logic;
74 signal Exception      : std_logic;
75
76 —Memory
77 signal mem_data_out   : std_logic_vector((DATA_WIDTH-1) downto 0);
78 signal mem_read       : std_logic;
79 signal addr_bus       : std_logic_vector((DATA_WIDTH-1) downto 0);
80 signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
81
82 begin
83     —Create a clock.
84     PROCESS
85     BEGIN
86         Clk <= '0';
87         WAIT FOR T/2;
88         Clk <= '1';
89         WAIT FOR T/2;
90     END PROCESS;
91
92     DUT: entity work.datapath
93     port map(
94         clk           => clk ,
95         PCWriteCondEq => PCWriteCondEq ,
96         PCWriteCondNEq => PCWriteCondNEq ,
97         PCWrite       => PCWrite ,
98         IorD          => IorD ,
99         MemRead       => MemRead ,
100        MemWrite      => MemWrite ,
101        MemToReg      => MemToReg ,
102        IRWrite       => IRWrite ,
103        RegWrite      => RegWrite ,
104        RegDst        => RegDst ,
105        ALUSrcA       => ALUSrcA ,
106        ALUSrcB       => ALUSrcB ,
107        PCSource      => PCSource ,
108        ALUOp         => ALUOp ,
109        UndefInstrEx  => UndefInstrEx ,
110        OverflowEx    => OverflowEx ,

```

```

111             Exception      => Exception ,
112
113             mem_data_out    => mem_data_out ,
114             mem_read         => mem_read ,
115             addr_bus         => addr_bus ,
116             mem_write_data   => mem_write_data
117         );
118
119     PROCESS
120     BEGIN
121         PCWriteCondEq <= '0';
122         PCWrite <= '0';
123         IorD <= IOD_PC;
124         MemRead <= '0';
125         MemWrite <= '0';
126         MemToReg <= MTR_ALUOUT;
127         IRWrite <= '0';
128         RegWrite <= '0';
129         RegDst <= RD_RT;
130         ALUSrcA <= ASA_PC;
131         ALUSrcB <= ASB_REGB;
132         PCSource <= PS_PCINC;
133         ALUOp <= AOP_AND;
134
135         —  $R[2] \leq R[0] + R[1]$ 
136         mem_data_out <= "000000" & "00000" & "00001" & "00010" & "00000" &
            "100000";
137         wait for T;
138
139         — IF
140         MemRead <= '1';
141         ALUSrcA <= ASA_PC;
142         IorD <= IOD_PC;
143         IRWrite <= '1';
144         ALUSrcB <= ASB_FOUR;
145         ALUOp <= AOP_ADD;
146         PCWrite <= '0';
147         PCSource <= PS_PCINC;
148         wait for T/2;
149         PCWrite <= '1';
150         wait for T/2;
151
152         — ID/Bra Calc
153         PCWrite <= '0';
154         MemRead <= '0';
155         IRWrite <= '0';
156         ALUSrcA <= ASA_PC;
157         ALUSrcB <= ASB_SEXTS;
158         PCSource <= PS_PCINC;
159         ALUOp <= AOP_ADD;
160         wait for T;
161
162         — Execute
163         ALUSrcA <= ASA_REG_A;
164         ALUSrcB <= ASB_REGB;
165         ALUOp <= AOP_ADD;
166         wait for T;
167

```

```

168
169      — Write Back
170      MemToReg <= MTR.ALUOUT;
171      RegDst <= RD.RD;
172      wait for T/2;
173      RegWrite <= '1';
174      wait for T/2;
175
176
177      END PROCESS;
178
179 end architecture ADD_Testbench_1;

```

Listing 7: ADD\_Testbench

---

```

1  —————
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : AND_Testbench.vhdl
5  — Creation Date  : 21/11/2009
6  — Description:
7  —
8  —————
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15
16 Entity AND_Testbench is
17
18 end entity;
19
20
21
22 Architecture AND_Testbench_1 of AND_Testbench is
23
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27     port(
28         clk                : in std_logic;
29     — Control Unit
30         PCWriteCondEq      : in std_logic;
31         PCWriteCondNEq     : in std_logic;
32         PCWrite             : in std_logic;
33         IorD                : in t_iord;
34         MemRead             : in std_logic;
35         MemWrite            : in std_logic;
36         MemToReg            : in t_memToReg;
37         IRWrite             : in std_logic;
38         RegWrite            : in std_logic;
39         RegDst              : in t_regDst;
40         ALUSrcA             : in t_aluSrcA;
41         ALUSrcB             : in t_aluSrcB;
42         PCSource            : in t_pcSrc;
43         ALUOp               : in t_aluOp;
44

```

```

45         UndefInstrEx  : in std_logic;
46         OverflowEx    : out std_logic;
47         Exception     : in std_logic;
48
49     —Memory
50     mem_data_out      : in  std_logic_vector((DATA_WIDTH-1) downto 0);
51     mem_read          : out std_logic;
52     addr_bus          : out std_logic_vector((DATA_WIDTH-1) downto 0);
53     mem_write_data    : out std_logic_vector((DATA_WIDTH-1) downto 0)
54 );
55 end component datapath;
56
57 signal PCWriteCondEq : std_logic;
58 signal PCWriteCondNEq : std_logic;
59 signal PCWrite       : std_logic;
60 signal IorD          : t_iord;
61 signal MemRead       : std_logic;
62 signal MemWrite      : std_logic;
63 signal MemToReg      : t_memToReg;
64 signal IRWrite       : std_logic;
65 signal RegWrite      : std_logic;
66 signal RegDst        : t_regDst;
67 signal ALUSrcA       : t_aluSrcA;
68 signal ALUSrcB       : t_aluSrcB;
69 signal PCSource      : t_pcSrc;
70 signal ALUOp         : t_aluOp;
71
72 signal UndefInstrEx  : std_logic;
73 signal OverflowEx    : std_logic;
74 signal Exception     : std_logic;
75
76 —Memory
77 signal mem_data_out  : std_logic_vector((DATA_WIDTH-1) downto 0);
78 signal mem_read      : std_logic;
79 signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);
80 signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
81
82 begin
83     —Create a clock.
84     PROCESS
85     BEGIN
86         Clk <= '0';
87         WAIT FOR T/2;
88         Clk <= '1';
89         WAIT FOR T/2;
90     END PROCESS;
91
92     DUT: entity work.datapath
93     port map(
94         clk           => clk ,
95         PCWriteCondEq => PCWriteCondEq,
96         PCWriteCondNEq => PCWriteCondNEq,
97         PCWrite       => PCWrite ,
98         IorD          => IorD ,
99         MemRead       => MemRead,
100        MemWrite      => MemWrite,
101        MemToReg      => MemToReg,
102        IRWrite       => IRWrite ,

```

```

103         RegWrite      => RegWrite ,
104         RegDst         => RegDst ,
105         ALUSrcA        => ALUSrcA ,
106         ALUSrcB        => ALUSrcB ,
107         PCSrc          => PCSrc ,
108         ALUOp          => ALUOp ,
109         UndefInstrEx   => UndefInstrEx ,
110         OverflowEx     => OverflowEx ,
111         Exception      => Exception ,
112
113         mem_data_out   => mem_data_out ,
114         mem_read        => mem_read ,
115         addr_bus        => addr_bus ,
116         mem_write_data => mem_write_data
117     );
118
119 PROCESS
120 BEGIN
121     PCWriteCondEq <= '0';
122     PCWrite <= '0';
123     IorD <= IOD_PC;
124     MemRead <= '0';
125     MemWrite <= '0';
126     MemToReg <= MTR_ALUOUT;
127     IRWrite <= '0';
128     RegWrite <= '0';
129     RegDst <= RD_RT;
130     ALUSrcA <= ASA_PC;
131     ALUSrcB <= ASB_REGB;
132     PCSrc <= PS_PCINC;
133     ALUOp <= AOP_AND;
134
135
136
137     —  $R[2] \leftarrow R[2] \text{ \& } R[1]$ 
138     mem_data_out <= "000000" & "00010" & "00001" & "00010" & "00000" &
        "100100";
139     wait for T;
140
141     — IF
142     MemRead <= '1';
143     ALUSrcA <= ASA_PC;
144     IorD <= IOD_PC;
145     IRWrite <= '1';
146     ALUSrcB <= ASB_FOUR;
147     ALUOp <= AOP_ADD;
148     PCWrite <= '0';
149     PCSrc <= PS_PCINC;
150     wait for T/2;
151     PCWrite <= '1';
152     wait for T/2;
153
154     — ID/Bra Calc
155     PCWrite <= '0';
156     MemRead <= '0';
157     IRWrite <= '0';
158     ALUSrcA <= ASA_PC;
159     ALUSrcB <= ASB_SEXTS;

```

```

160      PCSrc <= PS_PCINC;
161      ALUOp <= AOP_ADD;
162      wait for T;
163
164      — Execute
165      ALUSrcA <= ASA_REG_A;
166      ALUSrcB <= ASB_REGB;
167      ALUOp <= AOP_AND;
168      wait for T;
169
170
171      — Write Back
172      MemToReg <= MTR_ALUOUT;
173      RegDst <= RD_RD;
174      wait for T/2;
175      RegWrite <= '1';
176      wait for T/2;
177
178
179      END PROCESS;
180
181 end architecture AND_Testbench_1;

```

Listing 8: AND\_Testbench

---

```

1  —
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : BEQ_Testbench.vhdl
5  — Creation Date  : 21/11/2009
6  — Description:
7  —
8  —
9  —
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 —
16 Entity BEQ_Testbench is
17 —
18 end entity;
19
20
21 —
22 Architecture BEQ_Testbench_1 of BEQ_Testbench is
23 —
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27     port(
28         clk           : in std_logic;
29         — Control Unit
30         PCWriteCondEq : in std_logic;
31         PCWriteCondNEq : in std_logic;
32         PCWrite       : in std_logic;
33         IorD           : in t_iord;
34         MemRead        : in std_logic;

```

```

35         MemWrite      : in std_logic;
36         MemToReg       : in t_memToReg;
37         IRWrite        : in std_logic;
38         RegWrite       : in std_logic;
39         RegDst         : in t_regDst;
40         ALUSrcA        : in t_aluSrcA;
41         ALUSrcB        : in t_aluSrcB;
42         PCSource       : in t_pcSrc;
43         ALUOp          : in t_aluOp;
44         UndefInstrEx   : in std_logic;
45         OverflowEx     : out std_logic;
46         Exception      : in std_logic;
47
48     —Memory
49         mem_data_out    : in  std_logic_vector((DATA_WIDTH-1) downto 0);
50         mem_read        : out std_logic;
51         addr_bus        : out std_logic_vector((DATA_WIDTH-1) downto 0);
52         mem_write_data  : out std_logic_vector((DATA_WIDTH-1) downto 0)
53     );
54     end component datapath;
55
56     signal PCWriteCondEq : std_logic;
57     signal PCWriteCondNEq : std_logic;
58     signal PCWrite       : std_logic;
59     signal IorD          : t_iord;
60     signal MemRead       : std_logic;
61     signal MemWrite      : std_logic;
62     signal MemToReg      : t_memToReg;
63     signal IRWrite       : std_logic;
64     signal RegWrite      : std_logic;
65     signal RegDst        : t_regDst;
66     signal ALUSrcA       : t_aluSrcA;
67     signal ALUSrcB       : t_aluSrcB;
68     signal PCSource      : t_pcSrc;
69     signal ALUOp         : t_aluOp;
70     signal UndefInstrEx  : std_logic;
71     signal OverflowEx    : std_logic;
72     signal Exception     : std_logic;
73
74     —Memory
75     signal mem_data_out    : std_logic_vector((DATA_WIDTH-1) downto 0);
76     signal mem_read        : std_logic;
77     signal addr_bus        : std_logic_vector((DATA_WIDTH-1) downto 0);
78     signal mem_write_data  : std_logic_vector((DATA_WIDTH-1) downto 0);
79
80     begin
81         —Create a clock.
82         PROCESS
83             BEGIN
84                 Clk <= '0';
85                 WAIT FOR T/2;
86                 Clk <= '1';
87                 WAIT FOR T/2;
88             END PROCESS;
89
90         DUT: entity work.datapath
91             port map(
92                 clk          => clk ,

```



```

93         PCWriteCondEq => PCWriteCondEq ,
94         PCWriteCondNEq => PCWriteCondNEq ,
95         PCWrite        => PCWrite ,
96         IorD           => IorD ,
97         MemRead        => MemRead ,
98         MemWrite       => MemWrite ,
99         MemToReg       => MemToReg ,
100        IRWrite        => IRWrite ,
101        RegWrite       => RegWrite ,
102        RegDst         => RegDst ,
103        ALUSrcA        => ALUSrcA ,
104        ALUSrcB        => ALUSrcB ,
105        PCSource       => PCSource ,
106        ALUOp          => ALUOp ,
107        UndefInstrEx   => UndefInstrEx ,
108        OverflowEx     => OverflowEx ,
109        Exception      => Exception ,
110
111        mem_data_out   => mem_data_out ,
112        mem_read       => mem_read ,
113        addr_bus       => addr_bus ,
114        mem_write_data => mem_write_data
115    );
116
117    PROCESS
118    BEGIN
119        PCWriteCondEq <= '0';
120        PCWrite <= '0';
121        IorD <= IOD_PC;
122        MemRead <= '0';
123        MemWrite <= '0';
124        MemToReg <= MTR_ALUOUT;
125        IRWrite <= '0';
126        RegWrite <= '0';
127        RegDst <= RD_RT;
128        ALUSrcA <= ASA_PC;
129        ALUSrcB <= ASB_REGB;
130        PCSource <= PS_PCINC;
131        ALUOp <= AOP_AND;
132
133        — BEQ R1, R0, 8
134        mem_data_out <= "000100" & "00000" & "00001" & "00000000000000010";
135        wait for T;
136
137        — IF
138        MemRead <= '1';
139        ALUSrcA <= ASA_PC;
140        IorD <= IOD_PC;
141        IRWrite <= '1';
142        ALUSrcB <= ASB_FOUR;
143        ALUOp <= AOP_ADD;
144        PCWrite <= '0';
145        PCSource <= PS_PCINC;
146        wait for T/2;
147        PCWrite <= '1';
148        wait for T/2;
149
150        — ID/Bra Calc

```

```

151         PCWrite <= '0';
152         MemRead <= '0';
153         IRWrite <= '0';
154         ALUSrcA <= ASA_PC;
155         ALUSrcB <= ASB_SEXTS;
156         PCSource <= PS_PCINC;
157         ALUOp <= AOP_ADD;
158         wait for T;
159
160         — Branch Completion
161         ALUSrcA <= ASA_REG_A;
162         ALUSrcB <= ASB_REGB;
163         ALUOp <= AOP_SUB;
164         PCWriteCondEq <= '0';
165         PCSource <= PS_ALUOUT;
166         wait for T/2;
167         PCWriteCondEq <= '1';
168         wait for T/2;
169
170     END PROCESS;
171
172 end architecture BEQ_Testbench_1;

```

Listing 9: BEQ\_Testbench

---

```

1  —————
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : BNEQ_Testbench.vhdl
5  — Creation Date  : 21/11/2009
6  — Description:
7  —
8  —————
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips.lib.all;
14
15 —————
16 Entity BNEQ_Testbench is
17
18 end entity;
19
20
21 —————
22 Architecture BNEQ_Testbench_1 of BNEQ_Testbench is
23
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27         port(
28             clk           : in std_logic;
29             — Control Unit
30             PCWriteCondEq : in std_logic;
31             PCWrite       : in std_logic;
32             IorD          : in t_iord;
33             MemRead       : in std_logic;
34             MemWrite      : in std_logic;

```

```

35         MemToReg      : in t_memToReg;
36         IRWrite       : in std_logic;
37         RegWrite      : in std_logic;
38         RegDst        : in t_regDst;
39         ALUSrcA       : in t_aluSrcA;
40         ALUSrcB       : in t_aluSrcB;
41         PCSource      : in t_pcSrc;
42         ALUOp         : in t_aluOp;
43         UndefInstrEx  : in std_logic;
44         OverflowEx    : out std_logic;
45         Exception     : in std_logic;
46
47     —Memory
48     mem_data_out      : in  std_logic_vector((DATA_WIDTH-1) downto 0);
49     mem_read          : out std_logic;
50     addr_bus         : out std_logic_vector((DATA_WIDTH-1) downto 0);
51     mem_write_data    : out std_logic_vector((DATA_WIDTH-1) downto 0)
52 );
53 end component datapath;
54
55 signal PCWriteCondEq : std_logic;
56 signal PCWriteCondNEq : std_logic;
57 signal PCWrite       : std_logic;
58 signal IorD          : t_iord;
59 signal MemRead       : std_logic;
60 signal MemWrite      : std_logic;
61 signal MemToReg      : t_memToReg;
62 signal IRWrite       : std_logic;
63 signal RegWrite      : std_logic;
64 signal RegDst        : t_regDst;
65 signal ALUSrcA       : t_aluSrcA;
66 signal ALUSrcB       : t_aluSrcB;
67 signal PCSource      : t_pcSrc;
68 signal ALUOp         : t_aluOp;
69 signal UndefInstrEx  : std_logic;
70 signal OverflowEx    : std_logic;
71 signal Exception     : std_logic;
72 —Memory
73 signal mem_data_out  : std_logic_vector((DATA_WIDTH-1) downto 0);
74 signal mem_read      : std_logic;
75 signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);
76 signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
77
78 begin
79     —Create a clock.
80     PROCESS
81     BEGIN
82         Clk <= '0';
83         WAIT FOR T/2;
84         Clk <= '1';
85         WAIT FOR T/2;
86     END PROCESS;
87
88     DUT: entity work.datapath
89     port map(
90         clk           => clk ,
91         PCWriteCondEq => PCWriteCondEq,
92         PCWriteCondNEq => PCWriteCondNEq,

```

```

93         PCWrite      => PCWrite ,
94         IorD         => IorD ,
95         MemRead      => MemRead ,
96         MemWrite     => MemWrite ,
97         MemToReg     => MemToReg ,
98         IRWrite      => IRWrite ,
99         RegWrite     => RegWrite ,
100        RegDst       => RegDst ,
101        ALUSrcA      => ALUSrcA ,
102        ALUSrcB      => ALUSrcB ,
103        PCSrc       => PCSrc ,
104        ALUOp        => ALUOp ,
105
106        UndefInstrEx => UndefInstrEx ,
107        OverflowEx   => OverflowEx ,
108        Exception    => Exception ,
109
110        mem_data_out => mem_data_out ,
111        mem_read     => mem_read ,
112        addr_bus     => addr_bus ,
113        mem_write_data => mem_write_data
114    );
115
116    PROCESS
117    BEGIN
118        PCWriteCondEq <= '0';
119        PCWriteCondNEq <= '0';
120        PCWrite <= '0';
121        IorD <= IOD_PC;
122        MemRead <= '0';
123        MemWrite <= '0';
124        MemToReg <= MTR_ALUOUT;
125        IRWrite <= '0';
126        RegWrite <= '0';
127        RegDst <= RD_RT;
128        ALUSrcA <= ASA_PC;
129        ALUSrcB <= ASB_REGB;
130        PCSrc <= PS_PCINC;
131        ALUOp <= AOP_AND;
132
133        — BEQ R1, R0, 8
134        mem_data_out <= "000101" & "00000" & "00001" & "00000000000000010";
135        wait for T;
136
137        — IF
138        MemRead <= '1';
139        ALUSrcA <= ASA_PC;
140        IorD <= IOD_PC;
141        IRWrite <= '1';
142        ALUSrcB <= ASB_FOUR;
143        ALUOp <= AOP_ADD;
144        PCWrite <= '0';
145        PCSrc <= PS_PCINC;
146        wait for T/2;
147        PCWrite <= '1';
148        wait for T/2;
149
150        — ID/Bra Calc

```

```

151      PCWrite <= '0';
152      MemRead <= '0';
153      IRWrite <= '0';
154      ALUSrcA <= ASA_PC;
155      ALUSrcB <= ASB_SEXTS;
156      PCSource <= PS_PCINC;
157      ALUOp <= AOP_ADD;
158      wait for T;
159
160      — Branch Completion
161      ALUSrcA <= ASA_REG_A;
162      ALUSrcB <= ASB_REGB;
163      ALUOp <= AOP_SUB;
164      PCWriteCondNEq <= '0';
165      PCSource <= PS_ALUOUT;
166      wait for T/2;
167      PCWriteCondNEq <= '1';
168      wait for T/2;
169
170      END PROCESS;
171
172 end architecture BNEQ_Testbench_1;

```

Listing 10: BNEQ\_Testbench

---

```

1  —
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : IF_Testbench.vhdl
5  — Creation Date  : 21/11/2009
6  — Description:
7  —
8  —
9  —
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips.lib.all;
14
15 —
16 Entity IF_Testbench is
17 —
18 end entity;
19
20
21 —
22 Architecture IF_Testbench_1 of IF_Testbench is
23 —
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27     port(
28         clk           : in std_logic;
29         — Control Unit
30         PCWriteCondEq : in std_logic;
31         PCWriteCondNEq : in std_logic;
32         PCWrite        : in std_logic;
33         IorD            : in t_iord;
34         MemRead         : in std_logic;

```

```

35         MemWrite      : in std_logic;
36         MemToReg       : in t_memToReg;
37         IRWrite        : in std_logic;
38         RegWrite       : in std_logic;
39         RegDst         : in t_regDst;
40         ALUSrcA        : in t_aluSrcA;
41         ALUSrcB        : in t_aluSrcB;
42         PCSource       : in t_pcSrc;
43         ALUOp          : in t_aluOp;
44         UndefInstrEx   : in std_logic;
45         OverflowEx     : out std_logic;
46         Exception      : in std_logic;
47
48     —Memory
49     mem_data_out      : in  std_logic_vector((DATA_WIDTH-1) downto 0);
50     mem_read          : out std_logic;
51     addr_bus          : out std_logic_vector((DATA_WIDTH-1) downto 0);
52     mem_write_data    : out std_logic_vector((DATA_WIDTH-1) downto 0)
53 );
54 end component datapath;
55
56 signal PCWriteCondEq : std_logic;
57 signal PCWriteCondNEq : std_logic;
58 signal PCWrite        : std_logic;
59 signal IorD           : t_iord;
60 signal MemRead        : std_logic;
61 signal MemWrite       : std_logic;
62 signal MemToReg       : t_memToReg;
63 signal IRWrite        : std_logic;
64 signal RegWrite       : std_logic;
65 signal RegDst         : t_regDst;
66 signal ALUSrcA        : t_aluSrcA;
67 signal ALUSrcB        : t_aluSrcB;
68 signal PCSource       : t_pcSrc;
69 signal ALUOp          : t_aluOp;
70
71 signal UndefInstrEx   : std_logic;
72 signal OverflowEx     : std_logic;
73 signal Exception      : std_logic;
74
75
76 —Memory
77 signal mem_data_out    : std_logic_vector((DATA_WIDTH-1) downto 0);
78 signal mem_read        : std_logic;
79 signal addr_bus        : std_logic_vector((DATA_WIDTH-1) downto 0);
80 signal mem_write_data  : std_logic_vector((DATA_WIDTH-1) downto 0);
81
82 begin
83     —Create a clock.
84     PROCESS
85     BEGIN
86         Clk <= '0';
87         WAIT FOR T/2;
88         Clk <= '1';
89         WAIT FOR T/2;
90     END PROCESS;
91
92     DUT: entity work.datapath

```

```

93  port map(
94      clk                => clk ,
95      PCWriteCondEq      => PCWriteCondEq ,
96      PCWriteCondNEq     => PCWriteCondNEq ,
97      PCWrite            => PCWrite ,
98      IorD               => IorD ,
99      MemRead            => MemRead ,
100     MemWrite           => MemWrite ,
101     MemToReg           => MemToReg ,
102     IRWrite            => IRWrite ,
103     RegWrite           => RegWrite ,
104     RegDst             => RegDst ,
105     ALUSrcA            => ALUSrcA ,
106     ALUSrcB            => ALUSrcB ,
107     PCSrc              => PCSrc ,
108     ALUOp              => ALUOp ,
109     UndefInstrEx       => UndefInstrEx ,
110     OverflowEx         => OverflowEx ,
111     Exception          => Exception ,
112
113     mem_data_out        => mem_data_out ,
114     mem_read            => mem_read ,
115     addr_bus            => addr_bus ,
116     mem_write_data      => mem_write_data
117 );
118
119 PROCESS
120 BEGIN
121     PCWriteCondEq <= '0';
122     PCWrite <= '0';
123     IorD <= IOD_PC;
124     MemRead <= '0';
125     MemWrite <= '0';
126     MemToReg <= MTR_ALUOUT;
127     IRWrite <= '0';
128     RegWrite <= '0';
129     RegDst <= RD_RT;
130     ALUSrcA <= ASA_PC;
131     ALUSrcB <= ASB_REGB;
132     PCSrc <= PS_PCINC;
133     ALUOp <= AOP_AND;
134
135     --mem_data_out <= x"000000F0";
136     mem_data_out <= "00010000000000010000000000000010";
137     wait for T;
138
139     MemRead <= '1';
140     ALUSrcA <= ASA_PC;
141     IorD <= IOD_PC;
142     IRWrite <= '1';
143     ALUSrcB <= ASB_FOUR;
144     ALUOp <= AOP_ADD;
145     PCWrite <= '0';
146     PCSrc <= PS_PCINC;
147     wait for T/2;
148     PCWrite <= '1';
149     wait for T/2;
150     PCWrite <= '0';

```

```

151         MemRead <= '0';
152         IRWrite <= '0';
153         ALUSrcA <= ASA_PC;
154         ALUSrcB <= ASB_SEXTS;
155         PCSource <= PS_PCINC;
156         ALUOp <= AOP_ADD;
157         wait for T;
158
159     END PROCESS;
160
161 end architecture IF_Testbench_1;

```

Listing 11: IF\_Testbench

---

```

1  -----
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : JAL_Testbench.vhdl
5  — Creation Date  : 21/11/2009
6  — Description:
7  —
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 -----
16 Entity JAL_Testbench is
17
18 end entity;
19
20
21 -----
22 Architecture JAL_Testbench_1 of JAL_Testbench is
23 -----
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27         port(
28             clk                : in std_logic;
29             — Control Unit
30             PCWriteCondEq      : in std_logic;
31             PCWriteCondNEq     : in std_logic;
32             PCWrite             : in std_logic;
33             IorD                : in t_iord;
34             MemRead             : in std_logic;
35             MemWrite            : in std_logic;
36             MemToReg            : in t_memToReg;
37             IRWrite             : in std_logic;
38             RegWrite            : in std_logic;
39             RegDst              : in t_regDst;
40             ALUSrcA             : in t_aluSrcA;
41             ALUSrcB             : in t_aluSrcB;
42             PCSource            : in t_pcSrc;
43             ALUOp               : in t_aluOp;
44             UndefInstrEx        : in std_logic;
45             OverflowEx          : out std_logic;

```



```

46         Exception      : in std_logic;
47
48     —Memory
49         mem_data_out    : in  std_logic_vector((DATA_WIDTH-1) downto 0);
50         mem_read        : out std_logic;
51         addr_bus        : out std_logic_vector((DATA_WIDTH-1) downto 0);
52         mem_write_data  : out std_logic_vector((DATA_WIDTH-1) downto 0);
53     );
54     end component datapath;
55
56     signal PCWriteCondEq : std_logic;
57     signal PCWriteCondNEq : std_logic;
58     signal PCWrite       : std_logic;
59     signal IorD          : t_iord;
60     signal MemRead       : std_logic;
61     signal MemWrite      : std_logic;
62     signal MemToReg      : t_memToReg;
63     signal IRWrite       : std_logic;
64     signal RegWrite      : std_logic;
65     signal RegDst        : t_regDst;
66     signal ALUSrcA       : t_aluSrcA;
67     signal ALUSrcB       : t_aluSrcB;
68     signal PCSource      : t_pcSrc;
69     signal ALUOp         : t_aluOp;
70     signal UndefInstrEx  : std_logic;
71     signal OverflowEx    : std_logic;
72     signal Exception     : std_logic;
73     —Memory
74     signal mem_data_out  : std_logic_vector((DATA_WIDTH-1) downto 0);
75     signal mem_read      : std_logic;
76     signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);
77     signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
78
79     begin
80         —Create a clock.
81         PROCESS
82             BEGIN
83                 Clk <= '0';
84                 WAIT FOR T/2;
85                 Clk <= '1';
86                 WAIT FOR T/2;
87             END PROCESS;
88
89         DUT: entity work.datapath
90             port map(
91                 clk          => clk ,
92                 PCWriteCondEq => PCWriteCondEq ,
93                 PCWriteCondNEq => PCWriteCondNEq ,
94                 PCWrite      => PCWrite ,
95                 IorD         => IorD ,
96                 MemRead      => MemRead ,
97                 MemWrite     => MemWrite ,
98                 MemToReg     => MemToReg ,
99                 IRWrite      => IRWrite ,
100                RegWrite     => RegWrite ,
101                RegDst        => RegDst ,
102                ALUSrcA       => ALUSrcA ,
103                ALUSrcB       => ALUSrcB ,

```

```

104          PCSource          => PCSource ,
105          ALUOp             => ALUOp,
106          UndefInstrEx      => UndefInstrEx ,
107          OverflowEx        => OverflowEx ,
108          Exception         => Exception ,
109
110          mem_data_out      => mem_data_out ,
111          mem_read          => mem_read ,
112          addr_bus          => addr_bus ,
113          mem_write_data    => mem_write_data
114      );
115
116  PROCESS
117  BEGIN
118      PCWriteCondEq <= '0';
119      PCWriteCondNEq <= '0';
120      PCWrite <= '0';
121      IorD <= IOD_PC;
122      MemRead <= '0';
123      MemWrite <= '0';
124      MemToReg <= MTR_ALUOUT;
125      IRWrite <= '0';
126      RegWrite <= '0';
127      RegDst <= RD_RT;
128      ALUSrcA <= ASA_PC;
129      ALUSrcB <= ASB_REGB;
130      PCSource <= PS_PCINC;
131      ALUOp <= AOP_AND;
132
133      — BEQ R1, R0, 8
134      mem_data_out <= "000011" & "0000000000000000000000001000";
135      wait for T;
136
137      — IF
138      MemRead <= '1';
139      ALUSrcA <= ASA_PC;
140      IorD <= IOD_PC;
141      IRWrite <= '1';
142      ALUSrcB <= ASB_FOUR;
143      ALUOp <= AOP_ADD;
144      PCWrite <= '0';
145      PCSource <= PS_PCINC;
146      wait for T/2;
147      PCWrite <= '1';
148      wait for T/2;
149
150      — ID/Bra Calc
151      PCWrite <= '0';
152      MemRead <= '0';
153      IRWrite <= '0';
154      ALUSrcA <= ASA_PC;
155      ALUSrcB <= ASB_SEXTS;
156      PCSource <= PS_PCINC;
157      ALUOp <= AOP_ADD;
158      wait for T;
159
160      — Branch Completion
161      MemToReg <= MTR_PC;

```

```

162         RegDst <= RD_RA;
163         RegWrite <= '0';
164         PCWrite <= '0';
165         PCSource <= PS_JMP;
166         wait for T/2;
167         PCWrite <= '1';
168         RegWrite <= '1';
169         wait for T/2;
170
171     END PROCESS;
172
173 end architecture JAL_Testbench_1;

```

Listing 12: JAL\_Testbench

---

```

1  —————
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File          : J_Testbench.vhdl
5  — Creation Date : 21/11/2009
6  — Description :
7  —
8  —————
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 —————
16 Entity J_Testbench is
17
18 end entity;
19
20
21 —————
22 Architecture J_Testbench_1 of J_Testbench is
23
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27         port(
28             clk                : in std_logic;
29             — Control Unit
30             PCWriteCondEq      : in std_logic;
31             PCWriteCondNEq     : in std_logic;
32             PCWrite             : in std_logic;
33             IorD                : in t_iord;
34             MemRead             : in std_logic;
35             MemWrite            : in std_logic;
36             MemToReg            : in t_memToReg;
37             IRWrite             : in std_logic;
38             RegWrite            : in std_logic;
39             RegDst              : in t_regDst;
40             ALUSrcA             : in t_aluSrcA;
41             ALUSrcB             : in t_aluSrcB;
42             PCSource            : in t_pcSrc;
43             ALUOp               : in t_aluOp;
44             UndefInstrEx       : in std_logic;

```

```

45         OverflowEx      : out std_logic;
46         Exception       : in  std_logic;
47     —Memory
48         mem_data_out    : in  std_logic_vector((DATA_WIDTH-1) downto 0);
49         mem_read        : out std_logic;
50         addr_bus        : out std_logic_vector((DATA_WIDTH-1) downto 0);
51         mem_write_data  : out std_logic_vector((DATA_WIDTH-1) downto 0)
52     );
53     end component datapath;
54
55     signal PCWriteCondEq : std_logic;
56     signal PCWriteCondNEq : std_logic;
57     signal PCWrite       : std_logic;
58     signal IorD          : t_iord;
59     signal MemRead       : std_logic;
60     signal MemWrite      : std_logic;
61     signal MemToReg      : t_memToReg;
62     signal IRWrite       : std_logic;
63     signal RegWrite      : std_logic;
64     signal RegDst        : t_regDst;
65     signal ALUSrcA       : t_aluSrcA;
66     signal ALUSrcB       : t_aluSrcB;
67     signal PCSource      : t_pcSrc;
68     signal ALUOp         : t_aluOp;
69     signal UndefInstrEx  : std_logic;
70     signal OverflowEx    : std_logic;
71     signal Exception     : std_logic;
72     —Memory
73     signal mem_data_out   : std_logic_vector((DATA_WIDTH-1) downto 0);
74     signal mem_read      : std_logic;
75     signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);
76     signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
77
78     begin
79         —Create a clock.
80         PROCESS
81         BEGIN
82             Clk <= '0';
83             WAIT FOR T/2;
84             Clk <= '1';
85             WAIT FOR T/2;
86         END PROCESS;
87
88         DUT: entity work.datapath
89         port map(
90             clk           => clk ,
91             PCWriteCondEq => PCWriteCondEq ,
92             PCWriteCondNEq => PCWriteCondNEq ,
93             PCWrite       => PCWrite ,
94             IorD          => IorD ,
95             MemRead       => MemRead ,
96             MemWrite      => MemWrite ,
97             MemToReg      => MemToReg ,
98             IRWrite       => IRWrite ,
99             RegWrite      => RegWrite ,
100            RegDst        => RegDst ,
101            ALUSrcA       => ALUSrcA ,
102            ALUSrcB       => ALUSrcB ,

```



```

161         PCSource <= PS_JMP;
162         wait for T/2;
163         PCWrite <= '1';
164         wait for T/2;
165     END PROCESS;
166
167
168 end architecture J_Testbench_1;

```

Listing 13: J\_Testbench

```

1  -----
2  -- Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  --
4  -- File           : LW_Testbench.vhdl
5  -- Creation Date  : 21/11/2009
6  -- Description:
7  --
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 -----
16 Entity LW_Testbench is
17
18 end entity;
19
20
21 -----
22 Architecture LW_Testbench_1 of LW_Testbench is
23
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27         port(
28             clk                : in std_logic;
29             -- Control Unit
30             PCWriteCondEq      : in std_logic;
31             PCWriteCondNEq     : in std_logic;
32             PCWrite             : in std_logic;
33             IorD                : in t_iord;
34             MemRead             : in std_logic;
35             MemWrite            : in std_logic;
36             MemToReg            : in t_memToReg;
37             IRWrite             : in std_logic;
38             RegWrite            : in std_logic;
39             RegDst              : in t_regDst;
40             ALUSrcA             : in t_aluSrcA;
41             ALUSrcB             : in t_aluSrcB;
42             PCSource            : in t_pcSrc;
43             ALUOp               : in t_aluOp;
44             UndefInstrEx        : in std_logic;
45             OverflowEx          : out std_logic;
46             Exception           : in std_logic;
47             --Memory
48             mem_data_out        : in  std_logic_vector((DATA_WIDTH-1) downto 0);

```

```

49         mem_read          : out std_logic;
50         addr_bus          : out std_logic_vector((DATA_WIDTH-1) downto 0);
51         mem_write_data    : out std_logic_vector((DATA_WIDTH-1) downto 0)
52     );
53 end component datapath;
54
55 signal PCWriteCondEq : std_logic;
56 signal PCWriteCondNEq : std_logic;
57 signal PCWrite       : std_logic;
58 signal IorD          : t_iord;
59 signal MemRead       : std_logic;
60 signal MemWrite      : std_logic;
61 signal MemToReg      : t_memToReg;
62 signal IRWrite       : std_logic;
63 signal RegWrite      : std_logic;
64 signal RegDst        : t_regDst;
65 signal ALUSrcA       : t_aluSrcA;
66 signal ALUSrcB       : t_aluSrcB;
67 signal PCSource      : t_pcSrc;
68 signal ALUOp         : t_aluOp;
69 signal UndefInstrEx  : std_logic;
70 signal OverflowEx    : std_logic;
71 signal Exception     : std_logic;
72 —Memory
73 signal mem_data_out   : std_logic_vector((DATA_WIDTH-1) downto 0);
74 signal mem_read      : std_logic;
75 signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);
76 signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
77
78 begin
79     —Create a clock.
80     PROCESS
81     BEGIN
82         Clk <= '0';
83         WAIT FOR T/2;
84         Clk <= '1';
85         WAIT FOR T/2;
86     END PROCESS;
87
88     DUT: entity work.datapath
89     port map(
90         clk           => clk ,
91         PCWriteCondEq => PCWriteCondEq ,
92         PCWriteCondNEq => PCWriteCondNEq ,
93         PCWrite       => PCWrite ,
94         IorD          => IorD ,
95         MemRead       => MemRead ,
96         MemWrite      => MemWrite ,
97         MemToReg      => MemToReg ,
98         IRWrite       => IRWrite ,
99         RegWrite      => RegWrite ,
100        RegDst        => RegDst ,
101        ALUSrcA       => ALUSrcA ,
102        ALUSrcB       => ALUSrcB ,
103        PCSource      => PCSource ,
104        ALUOp         => ALUOp ,
105        UndefInstrEx  => UndefInstrEx ,
106        OverflowEx    => OverflowEx ,

```

```

107             Exception      => Exception ,
108
109             mem_data_out    => mem_data_out ,
110             mem_read        => mem_read ,
111             addr_bus        => addr_bus ,
112             mem_write_data  => mem_write_data
113         );
114
115     PROCESS
116     BEGIN
117         PCWriteCondEq <= '0';
118         PCWriteCondNEq <= '0';
119         PCWrite <= '0';
120         IorD <= IOD_PC;
121         MemRead <= '0';
122         MemWrite <= '0';
123         MemToReg <= MTR_ALUOUT;
124         IRWrite <= '0';
125         RegWrite <= '0';
126         RegDst <= RD_RT;
127         ALUSrcA <= ASA_PC;
128         ALUSrcB <= ASB_REGB;
129         PCSrc <= PS_PCINC;
130         ALUOp <= AOP_AND;
131
132         —  $R[1] \leq R0 + 4$ 
133         mem_data_out <= "100011" & "00000" & "00001" & x"00FF";
134         wait for T;
135
136         — IF
137         MemRead <= '1';
138         ALUSrcA <= ASA_PC;
139         IorD <= IOD_PC;
140         IRWrite <= '1';
141         ALUSrcB <= ASB_FOUR;
142         ALUOp <= AOP_ADD;
143         PCWrite <= '0';
144         PCSrc <= PS_PCINC;
145         wait for T/2;
146         PCWrite <= '1';
147         wait for T/2;
148         — ID/Bra Calc
149         PCWrite <= '0';
150         MemRead <= '0';
151         IRWrite <= '0';
152         ALUSrcA <= ASA_PC;
153         ALUSrcB <= ASB_SEXTS;
154         PCSrc <= PS_PCINC;
155         ALUOp <= AOP_ADD;
156         wait for T;
157
158         — Memory Address Comp
159         ALUSrcA <= ASA_REG_A;
160         ALUSrcB <= ASB_SEXT;
161         ALUOp <= AOP_ADD;
162         wait for T;
163
164         — Memory Access

```



```

165         IorD <= IOD_ALUOUT;
166         MemRead <= '1';
167         wait for T/2;
168         MemRead <= '0';
169         wait for T/2;
170
171         — Write Back
172         MemToReg <= MTR_MDR;
173         RegDst <= RD_RT;
174         wait for T/2;
175         RegWrite <= '1';
176         wait for T/2;
177
178
179     END PROCESS;
180
181 end architecture LW_Testbench_1;

```

Listing 14: LW\_Testbench

---

```

1  —————
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : OR_Testbench.vhdl
5  — Creation Date  : 21/11/2009
6  — Description:
7  —
8  —————
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 —————
16 Entity OR_Testbench is
17 —————
18 end entity;
19
20
21 —————
22 Architecture OR_Testbench_1 of OR_Testbench is
23 —————
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27         port(
28             clk           : in std_logic;
29             — Control Unit
30             PCWriteCondEq : in std_logic;
31             PCWriteCondNEq : in std_logic;
32             PCWrite        : in std_logic;
33             IorD            : in t_iord;
34             MemRead        : in std_logic;
35             MemWrite       : in std_logic;
36             MemToReg       : in t_memToReg;
37             IRWrite        : in std_logic;
38             RegWrite       : in std_logic;
39             RegDst         : in t_regDst;

```

```

40         ALUSrcA      : in t_aluSrcA;
41         ALUSrcB      : in t_aluSrcB;
42         PCSource     : in t_pcSrc;
43         ALUOp        : in t_aluOp;
44         UndefInstrEx : in std_logic;
45         OverflowEx    : out std_logic;
46         Exception     : in std_logic;
47     —Memory
48     mem_data_out      : in  std_logic_vector((DATA_WIDTH-1) downto 0);
49     mem_read          : out std_logic;
50     addr_bus          : out std_logic_vector((DATA_WIDTH-1) downto 0);
51     mem_write_data    : out std_logic_vector((DATA_WIDTH-1) downto 0);
52 );
53 end component datapath;
54
55 signal PCWriteCondEq : std_logic;
56 signal PCWriteCondNEq : std_logic;
57 signal PCWrite       : std_logic;
58 signal IorD          : t_iord;
59 signal MemRead       : std_logic;
60 signal MemWrite      : std_logic;
61 signal MemToReg      : t_memToReg;
62 signal IRWrite       : std_logic;
63 signal RegWrite      : std_logic;
64 signal RegDst        : t_regDst;
65 signal ALUSrcA       : t_aluSrcA;
66 signal ALUSrcB       : t_aluSrcB;
67 signal PCSource      : t_pcSrc;
68 signal ALUOp         : t_aluOp;
69
70 signal UndefInstrEx  : std_logic;
71 signal OverflowEx    : std_logic;
72 signal Exception     : std_logic;
73 —Memory
74 signal mem_data_out  : std_logic_vector((DATA_WIDTH-1) downto 0);
75 signal mem_read      : std_logic;
76 signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);
77 signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
78
79 begin
80     —Create a clock.
81     PROCESS
82     BEGIN
83         Clk <= '0';
84         WAIT FOR T/2;
85         Clk <= '1';
86         WAIT FOR T/2;
87     END PROCESS;
88
89     DUT: entity work.datapath
90     port map(
91         clk           => clk ,
92         PCWriteCondEq => PCWriteCondEq,
93         PCWriteCondNEq => PCWriteCondNEq,
94         PCWrite       => PCWrite ,
95         IorD          => IorD ,
96         MemRead       => MemRead,
97         MemWrite      => MemWrite,

```

```

98         MemToReg      => MemToReg,
99         IRWrite       => IRWrite ,
100        RegWrite      => RegWrite ,
101        RegDst        => RegDst ,
102        ALUSrcA       => ALUSrcA ,
103        ALUSrcB       => ALUSrcB ,
104        PCSource      => PCSource ,
105        ALUOp         => ALUOp,
106        UndefInstrEx  => UndefInstrEx ,
107        OverflowEx    => OverflowEx ,
108        Exception     => Exception ,
109
110        mem_data_out   => mem_data_out ,
111        mem_read       => mem_read ,
112        addr_bus       => addr_bus ,
113        mem_write_data => mem_write_data
114    );
115
116    PROCESS
117    BEGIN
118        PCWriteCondEq <= '0';
119        PCWrite <= '0';
120        IorD <= IOD_PC;
121        MemRead <= '0';
122        MemWrite <= '0';
123        MemToReg <= MTR_ALUOUT;
124        IRWrite <= '0';
125        RegWrite <= '0';
126        RegDst <= RD_RT;
127        ALUSrcA <= ASA_PC;
128        ALUSrcB <= ASB_REGB;
129        PCSource <= PS_PCINC;
130        ALUOp <= AOP_AND;
131
132        —  $R[2] \leq R[2] \mid R[1]$ 
133        mem_data_out <= "000000" & "00010" & "00001" & "00010" & "00000" &
            "100101";
134        wait for T;
135
136        — IF
137        MemRead <= '1';
138        ALUSrcA <= ASA_PC;
139        IorD <= IOD_PC;
140        IRWrite <= '1';
141        ALUSrcB <= ASB_FOUR;
142        ALUOp <= AOP_ADD;
143        PCWrite <= '0';
144        PCSource <= PS_PCINC;
145        wait for T/2;
146        PCWrite <= '1';
147        wait for T/2;
148
149        — ID/Bra Calc
150        PCWrite <= '0';
151        MemRead <= '0';
152        IRWrite <= '0';
153        ALUSrcA <= ASA_PC;
154        ALUSrcB <= ASB_SEXTS;

```

```

155     PCSrc <= PS_PCINC;
156     ALUOp <= AOP_ADD;
157     wait for T;
158
159     — Execute
160     ALUSrcA <= ASA_REG_A;
161     ALUSrcB <= ASB_REGB;
162     ALUOp <= AOP_OR;
163     wait for T;
164
165     — Write Back
166     MemToReg <= MTR_ALUOUT;
167     RegDst <= RD_RD;
168     wait for T/2;
169     RegWrite <= '1';
170     wait for T/2;
171
172
173
174     END PROCESS;
175
176 end architecture OR_Testbench_1;

```

Listing 15: OR\_Testbench

```

1  -----
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : SLL_Testbench.vhdl
5  — Creation Date  : 21/11/2009
6  — Description:
7  —
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 -----
16 Entity SLL_Testbench is
17
18 end entity;
19
20
21 -----
22 Architecture SLL_Testbench_1 of SLL_Testbench is
23
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27     port(
28         clk           : in std_logic;
29     — Control Unit
30         PCWriteCondEq : in std_logic;
31         PCWriteCondNEq : in std_logic;
32         PCWrite       : in std_logic;
33         IorD           : in t_iord;
34         MemRead       : in std_logic;

```

```

35         MemWrite      : in std_logic;
36         MemToReg       : in t_memToReg;
37         IRWrite        : in std_logic;
38         RegWrite       : in std_logic;
39         RegDst         : in t_regDst;
40         ALUSrcA        : in t_aluSrcA;
41         ALUSrcB        : in t_aluSrcB;
42         PCSource       : in t_pcSrc;
43         ALUOp          : in t_aluOp;
44         UndefInstrEx   : in std_logic;
45         OverflowEx     : out std_logic;
46         Exception      : in std_logic;
47     —Memory
48         mem_data_out    : in std_logic_vector((DATA_WIDTH-1) downto 0);
49         mem_read        : out std_logic;
50         addr_bus        : out std_logic_vector((DATA_WIDTH-1) downto 0);
51         mem_write_data  : out std_logic_vector((DATA_WIDTH-1) downto 0)
52     );
53     end component datapath;
54
55     signal PCWriteCondEq : std_logic;
56     signal PCWriteCondNEq : std_logic;
57     signal PCWrite       : std_logic;
58     signal IorD          : t_iord;
59     signal MemRead       : std_logic;
60     signal MemWrite      : std_logic;
61     signal MemToReg      : t_memToReg;
62     signal IRWrite       : std_logic;
63     signal RegWrite      : std_logic;
64     signal RegDst        : t_regDst;
65     signal ALUSrcA       : t_aluSrcA;
66     signal ALUSrcB       : t_aluSrcB;
67     signal PCSource      : t_pcSrc;
68     signal ALUOp         : t_aluOp;
69     signal UndefInstrEx  : std_logic;
70     signal OverflowEx    : std_logic;
71     signal Exception     : std_logic;
72     —Memory
73     signal mem_data_out  : std_logic_vector((DATA_WIDTH-1) downto 0);
74     signal mem_read      : std_logic;
75     signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);
76     signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
77
78     begin
79         —Create a clock.
80         PROCESS
81             BEGIN
82                 Clk <= '0';
83                 WAIT FOR T/2;
84                 Clk <= '1';
85                 WAIT FOR T/2;
86             END PROCESS;
87
88         DUT: entity work.datapath
89             port map(
90                 clk          => clk ,
91                 PCWriteCondEq => PCWriteCondEq,
92                 PCWriteCondNEq => PCWriteCondNEq,

```

```

93         PCWrite      => PCWrite ,
94         IorD          => IorD ,
95         MemRead       => MemRead ,
96         MemWrite      => MemWrite ,
97         MemToReg      => MemToReg ,
98         IRWrite       => IRWrite ,
99         RegWrite      => RegWrite ,
100        RegDst        => RegDst ,
101        ALUSrcA        => ALUSrcA ,
102        ALUSrcB        => ALUSrcB ,
103        PCSrc          => PCSrc ,
104        ALUOp          => ALUOp ,
105        UndefInstrEx   => UndefInstrEx ,
106        OverflowEx     => OverflowEx ,
107        Exception      => Exception ,
108
109        mem_data_out    => mem_data_out ,
110        mem_read        => mem_read ,
111        addr_bus        => addr_bus ,
112        mem_write_data  => mem_write_data
113    );
114
115    PROCESS
116    BEGIN
117        PCWriteCondEq <= '0';
118        PCWriteCondNEq <= '0';
119        PCWrite <= '0';
120        IorD <= IOD_PC;
121        MemRead <= '0';
122        MemWrite <= '0';
123        MemToReg <= MTR_ALUOUT;
124        IRWrite <= '0';
125        RegWrite <= '0';
126        RegDst <= RD_RT;
127        ALUSrcA <= ASA_PC;
128        ALUSrcB <= ASB_REGB;
129        PCSrc <= PS_PCINC;
130        ALUOp <= AOP_AND;
131
132        —  $R[2] \leq R[1] < 2$ 
133        mem_data_out <= "000000" & "00000" & "00001" & "00010" & "00010" &
            "000000";
134        wait for T;
135
136        — IF
137        MemRead <= '1';
138        ALUSrcA <= ASA_PC;
139        IorD <= IOD_PC;
140        IRWrite <= '1';
141        ALUSrcB <= ASB_FOUR;
142        ALUOp <= AOP_ADD;
143        PCWrite <= '0';
144        PCSrc <= PS_PCINC;
145        wait for T/2;
146        PCWrite <= '1';
147        wait for T/2;
148
149        — ID/Bra Calc

```

```

150      PCWrite <= '0';
151      MemRead <= '0';
152      IRWrite <= '0';
153      ALUSrcA <= ASA_PC;
154      ALUSrcB <= ASB_SEXTS;
155      PCSrc <= PS_PCINC;
156      ALUOp <= AOP_ADD;
157      wait for T;
158
159      — Execute
160      ALUSrcA <= ASA_REG_A;
161      ALUSrcB <= ASB_REGB;
162      ALUOp <= AOP_SLL;
163      wait for T;
164
165      — Write Back
166      MemToReg <= MTR_ALUOUT;
167      RegDst <= RD_RD;
168      wait for T/2;
169      RegWrite <= '1';
170      wait for T/2;
171
172
173
174      END PROCESS;
175
176 end architecture SLL_Testbench_1;

```

Listing 16: SLL\_Testbench

```

1  —————
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : SLT_Testbench.vhdl
5  — Creation Date : 21/11/2009
6  — Description :
7  —
8  —————
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips_lib.all;
14
15 —————
16 Entity SLT_Testbench is
17 —————
18 end entity;
19
20
21 —————
22 Architecture SLT_Testbench_1 of SLT_Testbench is
23 —————
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27         port(
28             clk           : in std_logic;
29             — Control Unit

```

```

30         PCWriteCondEq : in std_logic;
31         PCWriteCondNEq : in std_logic;
32         PCWrite        : in std_logic;
33         IorD           : in t_iord;
34         MemRead        : in std_logic;
35         MemWrite       : in std_logic;
36         MemToReg       : in t_memToReg;
37         IRWrite        : in std_logic;
38         RegWrite       : in std_logic;
39         RegDst         : in t_regDst;
40         ALUSrcA        : in t_aluSrcA;
41         ALUSrcB        : in t_aluSrcB;
42         PCSource       : in t_pcSrc;
43         ALUOp          : in t_aluOp;
44
45         UndefInstrEx   : in std_logic;
46         OverflowEx     : out std_logic;
47         Exception      : in std_logic;
48     —Memory
49         mem_data_out    : in  std_logic_vector((DATA_WIDTH-1) downto 0);
50         mem_read        : out std_logic;
51         addr_bus        : out std_logic_vector((DATA_WIDTH-1) downto 0);
52         mem_write_data  : out std_logic_vector((DATA_WIDTH-1) downto 0)
53     );
54     end component datapath;
55
56     signal PCWriteCondEq : std_logic;
57     signal PCWriteCondNEq : std_logic;
58     signal PCWrite       : std_logic;
59     signal IorD          : t_iord;
60     signal MemRead       : std_logic;
61     signal MemWrite      : std_logic;
62     signal MemToReg      : t_memToReg;
63     signal IRWrite       : std_logic;
64     signal RegWrite      : std_logic;
65     signal RegDst        : t_regDst;
66     signal ALUSrcA       : t_aluSrcA;
67     signal ALUSrcB       : t_aluSrcB;
68     signal PCSource      : t_pcSrc;
69     signal ALUOp         : t_aluOp;
70
71     signal UndefInstrEx   : std_logic;
72     signal OverflowEx     : std_logic;
73     signal Exception      : std_logic;
74     —Memory
75     signal mem_data_out    : std_logic_vector((DATA_WIDTH-1) downto 0);
76     signal mem_read        : std_logic;
77     signal addr_bus        : std_logic_vector((DATA_WIDTH-1) downto 0);
78     signal mem_write_data  : std_logic_vector((DATA_WIDTH-1) downto 0);
79
80     begin
81         —Create a clock.
82         PROCESS
83             BEGIN
84                 Clk <= '0';
85                 WAIT FOR T/2;
86                 Clk <= '1';
87                 WAIT FOR T/2;

```



```

88  END PROCESS;
89
90  DUT: entity work.datapath
91  port map(
92      clk           => clk ,
93      PCWriteCondEq => PCWriteCondEq ,
94      PCWriteCondNEq => PCWriteCondNEq ,
95      PCWrite       => PCWrite ,
96      IorD          => IorD ,
97      MemRead       => MemRead ,
98      MemWrite      => MemWrite ,
99      MemToReg      => MemToReg ,
100     IRWrite       => IRWrite ,
101     RegWrite      => RegWrite ,
102     RegDst        => RegDst ,
103     ALUSrcA       => ALUSrcA ,
104     ALUSrcB       => ALUSrcB ,
105     PCSrc         => PCSrc ,
106     ALUOp         => ALUOp ,
107     UndefInstrEx  => UndefInstrEx ,
108     OverflowEx    => OverflowEx ,
109     Exception     => Exception ,
110
111     mem_data_out   => mem_data_out ,
112     mem_read       => mem_read ,
113     addr_bus       => addr_bus ,
114     mem_write_data => mem_write_data
115 );
116
117 PROCESS
118 BEGIN
119     PCWriteCondEq <= '0';
120     PCWrite <= '0';
121     IorD <= IOD_PC;
122     MemRead <= '0';
123     MemWrite <= '0';
124     MemToReg <= MTR_ALUOUT;
125     IRWrite <= '0';
126     RegWrite <= '0';
127     RegDst <= RD_RT;
128     ALUSrcA <= ASA_PC;
129     ALUSrcB <= ASB_REGB;
130     PCSrc <= PS_PCINC;
131     ALUOp <= AOP_AND;
132
133     —  $R[2] \leftarrow R[2] \& R[1]$ 
134     mem_data_out <= "000000" & "00010" & "00001" & "00010" & "00000" &
        "101010";
135     wait for T;
136
137     — IF
138     MemRead <= '1';
139     ALUSrcA <= ASA_PC;
140     IorD <= IOD_PC;
141     IRWrite <= '1';
142     ALUSrcB <= ASB_FOUR;
143     ALUOp <= AOP_ADD;
144     PCWrite <= '0';

```

```

145      PCSource <= PS_PCINC;
146      wait for T/2;
147      PCWrite <= '1';
148      wait for T/2;
149
150      — ID/Bra Calc
151      PCWrite <= '0';
152      MemRead <= '0';
153      IRWrite <= '0';
154      ALUSrcA <= ASA_PC;
155      ALUSrcB <= ASB_SEXTS;
156      PCSource <= PS_PCINC;
157      ALUOp <= AOP_ADD;
158      wait for T;
159
160      — Execute
161      ALUSrcA <= ASA_REG_A;
162      ALUSrcB <= ASB_REGB;
163      ALUOp <= AOP_SLT;
164      wait for T;
165
166
167      — Write Back
168      MemToReg <= MTR_ALUOUT;
169      RegDst <= RD_RD;
170      wait for T/2;
171      RegWrite <= '1';
172      wait for T/2;
173
174
175      END PROCESS;
176
177 end architecture SLT_Testbench_1;

```

Listing 17: SLT\_Testbench

---

```

1  —
2  — Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  —
4  — File           : SUB_Testbench.vhdl
5  — Creation Date  : 21/11/2009
6  — Description:
7  —
8  —
9  —
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips.lib.all;
14
15 —
16 Entity SUB_Testbench is
17 —
18 end entity;
19
20
21 —
22 Architecture SUB_Testbench_1 of SUB_Testbench is
23 —

```

---

```

24  constant T: time := 100 ns;
25  signal Clk : std_logic := '0';
26  component datapath
27      port(
28          clk          : in std_logic;
29  — Control Unit
30          PCWriteCondEq : in std_logic;
31          PCWriteCondNEq : in std_logic;
32          PCWrite       : in std_logic;
33          IorD          : in t_iord;
34          MemRead       : in std_logic;
35          MemWrite      : in std_logic;
36          MemToReg      : in t_memToReg;
37          IRWrite       : in std_logic;
38          RegWrite      : in std_logic;
39          RegDst        : in t_regDst;
40          ALUSrcA       : in t_aluSrcA;
41          ALUSrcB       : in t_aluSrcB;
42          PCSource      : in t_pcSrc;
43          ALUOp         : in t_aluOp;
44          UndefInstrEx  : in std_logic;
45          OverflowEx    : out std_logic;
46          Exception     : in std_logic;
47  —Memory
48          mem_data_out  : in  std_logic_vector((DATA_WIDTH-1) downto 0);
49          mem_read      : out std_logic;
50          addr_bus      : out std_logic_vector((DATA_WIDTH-1) downto 0);
51          mem_write_data : out std_logic_vector((DATA_WIDTH-1) downto 0)
52      );
53  end component datapath;
54
55  signal PCWriteCondEq : std_logic;
56  signal PCWriteCondNEq : std_logic;
57  signal PCWrite       : std_logic;
58  signal IorD          : t_iord;
59  signal MemRead       : std_logic;
60  signal MemWrite      : std_logic;
61  signal MemToReg      : t_memToReg;
62  signal IRWrite       : std_logic;
63  signal RegWrite      : std_logic;
64  signal RegDst        : t_regDst;
65  signal ALUSrcA       : t_aluSrcA;
66  signal ALUSrcB       : t_aluSrcB;
67  signal PCSource      : t_pcSrc;
68  signal ALUOp         : t_aluOp;
69  signal UndefInstrEx  : std_logic;
70  signal OverflowEx    : std_logic;
71  signal Exception     : std_logic;
72  —Memory
73  signal mem_data_out  : std_logic_vector((DATA_WIDTH-1) downto 0);
74  signal mem_read      : std_logic;
75  signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);
76  signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
77
78  begin
79  — Create a clock.
80  PROCESS
81  BEGIN

```

```

82         Clk <= '0';
83         WAIT FOR T/2;
84         Clk <= '1';
85         WAIT FOR T/2;
86     END PROCESS;
87
88     DUT: entity work.datapath
89     port map(
90         clk           => clk ,
91         PCWriteCondEq => PCWriteCondEq ,
92         PCWriteCondNEq => PCWriteCondNEq ,
93         PCWrite       => PCWrite ,
94         IorD          => IorD ,
95         MemRead       => MemRead ,
96         MemWrite      => MemWrite ,
97         MemToReg      => MemToReg ,
98         IRWrite       => IRWrite ,
99         RegWrite      => RegWrite ,
100        RegDst        => RegDst ,
101        ALUSrcA       => ALUSrcA ,
102        ALUSrcB       => ALUSrcB ,
103        PCSrc         => PCSrc ,
104        ALUOp         => ALUOp ,
105        UndefInstrEx  => UndefInstrEx ,
106        OverflowEx    => OverflowEx ,
107        Exception     => Exception ,
108
109        mem_data_out  => mem_data_out ,
110        mem_read      => mem_read ,
111        addr_bus      => addr_bus ,
112        mem_write_data => mem_write_data
113    );
114
115     PROCESS
116     BEGIN
117         PCWriteCondEq <= '0';
118         PCWrite <= '0';
119         IorD <= IOD_PC;
120         MemRead <= '0';
121         MemWrite <= '0';
122         MemToReg <= MTR_ALUOUT;
123         IRWrite <= '0';
124         RegWrite <= '0';
125         RegDst <= RD_RT;
126         ALUSrcA <= ASA_PC;
127         ALUSrcB <= ASB_REGB;
128         PCSrc <= PS_PCINC;
129         ALUOp <= AOP_AND;
130
131         —  $R[2] \leq R[0] - R[1]$ 
132         mem_data_out <= "000000" & "00000" & "00001" & "00010" & "00000" &
            "100010";
133         wait for T;
134
135         —  $IF$ 
136         MemRead <= '1';
137         ALUSrcA <= ASA_PC;
138         IorD <= IOD_PC;

```

```

139         IRWrite <= '1';
140         ALUSrcB <= ASB_FOUR;
141         ALUOp <= AOP_ADD;
142         PCWrite <= '0';
143         PCSrc <= PS_PCINC;
144         wait for T/2;
145         PCWrite <= '1';
146         wait for T/2;
147
148         -- ID/Bra Calc
149         PCWrite <= '0';
150         MemRead <= '0';
151         IRWrite <= '0';
152         ALUSrcA <= ASA_PC;
153         ALUSrcB <= ASB_SEXTS;
154         PCSrc <= PS_PCINC;
155         ALUOp <= AOP_ADD;
156         wait for T;
157
158         -- Execute
159         ALUSrcA <= ASA_REG_A;
160         ALUSrcB <= ASB_REGB;
161         ALUOp <= AOP_SUB;
162         wait for T;
163
164
165         -- Write Back
166         MemToReg <= MTR_ALUOUT;
167         RegDst <= RD_RD;
168         wait for T/2;
169         RegWrite <= '1';
170         wait for T/2;
171
172
173     END PROCESS;
174
175 end architecture SUB_Testbench_1;

```

Listing 18: SUB\_Testbench

---

```

1  --
2  -- Author(s)      : Jay Mundrawala <mundra@ir.iit.edu>
3  --
4  -- File           : SW_Testbench.vhdl
5  -- Creation Date  : 21/11/2009
6  -- Description:
7  --
8  --

```

---

```

9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.numeric_std.all;
13 use work.mips.lib.all;
14
15
16 Entity SW_Testbench is
17
18 end entity;
19

```

---

```

20
21
22 Architecture SW_Testbench_1 of SW_Testbench is
23
24     constant T: time := 100 ns;
25     signal Clk : std_logic := '0';
26     component datapath
27     port(
28         clk           : in std_logic;
29     — Control Unit
30         PCWriteCondEq : in std_logic;
31         PCWriteCondNEq : in std_logic;
32         PCWrite       : in std_logic;
33         IorD          : in t_iord;
34         MemRead       : in std_logic;
35         MemWrite      : in std_logic;
36         MemToReg      : in t_memToReg;
37         IRWrite       : in std_logic;
38         RegWrite      : in std_logic;
39         RegDst        : in t_regDst;
40         ALUSrcA       : in t_aluSrcA;
41         ALUSrcB       : in t_aluSrcB;
42         PCSrc         : in t_pcSrc;
43         ALUOp         : in t_aluOp;
44         UndefInstrEx  : in std_logic;
45         OverflowEx    : out std_logic;
46         Exception     : in std_logic;
47
48     — Memory
49         mem_data_out  : in std_logic_vector((DATA_WIDTH-1) downto 0);
50         mem_read      : out std_logic;
51         addr_bus      : out std_logic_vector((DATA_WIDTH-1) downto 0);
52         mem_write_data : out std_logic_vector((DATA_WIDTH-1) downto 0)
53     );
54 end component datapath;
55
56     signal PCWriteCondEq : std_logic;
57     signal PCWriteCondNEq : std_logic;
58     signal PCWrite       : std_logic;
59     signal IorD          : t_iord;
60     signal MemRead       : std_logic;
61     signal MemWrite      : std_logic;
62     signal MemToReg      : t_memToReg;
63     signal IRWrite       : std_logic;
64     signal RegWrite      : std_logic;
65     signal RegDst        : t_regDst;
66     signal ALUSrcA       : t_aluSrcA;
67     signal ALUSrcB       : t_aluSrcB;
68     signal PCSrc         : t_pcSrc;
69     signal ALUOp         : t_aluOp;
70
71     signal UndefInstrEx  : std_logic;
72     signal OverflowEx    : std_logic;
73     signal Exception     : std_logic;
74     — Memory
75     signal mem_data_out  : std_logic_vector((DATA_WIDTH-1) downto 0);
76     signal mem_read      : std_logic;
77     signal addr_bus      : std_logic_vector((DATA_WIDTH-1) downto 0);

```

```

78     signal mem_write_data : std_logic_vector((DATA_WIDTH-1) downto 0);
79
80 begin
81     — Create a clock.
82     PROCESS
83     BEGIN
84         Clk <= '0';
85         WAIT FOR T/2;
86         Clk <= '1';
87         WAIT FOR T/2;
88     END PROCESS;
89
90     DUT: entity work.datapath
91     port map(
92         clk           => clk ,
93         PCWriteCondEq => PCWriteCondEq ,
94         PCWriteCondNEq => PCWriteCondNEq ,
95         PCWrite       => PCWrite ,
96         IorD          => IorD ,
97         MemRead       => MemRead ,
98         MemWrite      => MemWrite ,
99         MemToReg      => MemToReg ,
100        IRWrite       => IRWrite ,
101        RegWrite      => RegWrite ,
102        RegDst        => RegDst ,
103        ALUSrcA       => ALUSrcA ,
104        ALUSrcB       => ALUSrcB ,
105        PCSrc         => PCSrc ,
106        ALUOp         => ALUOp ,
107        UndefInstrEx  => UndefInstrEx ,
108        OverflowEx    => OverflowEx ,
109        Exception     => Exception ,
110
111        mem_data_out  => mem_data_out ,
112        mem_read      => mem_read ,
113        addr_bus      => addr_bus ,
114        mem_write_data => mem_write_data
115    );
116
117     PROCESS
118     BEGIN
119         PCWriteCondEq <= '0';
120         PCWrite <= '0';
121         IorD <= IOD_PC;
122         MemRead <= '0';
123         MemWrite <= '0';
124         MemToReg <= MTR_ALUOUT;
125         IRWrite <= '0';
126         RegWrite <= '0';
127         RegDst <= RD_RT;
128         ALUSrcA <= ASA_PC;
129         ALUSrcB <= ASB_REGB;
130         PCSrc <= PS_PCINC;
131         ALUOp <= AOP_AND;
132
133         —  $R[1] \leq R0 + 4$ 
134         mem_data_out <= "101011" & "00000" & "00001" & x"00FF";
135         wait for T;

```

```

136
137      — IF
138      MemRead <= '1';
139      ALUSrcA <= ASA_PC;
140      IorD <= IOD_PC;
141      IRWrite <= '1';
142      ALUSrcB <= ASB_FOUR;
143      ALUOp <= AOP_ADD;
144      PCWrite <= '0';
145      PCSrc <= PS_PCINC;
146      wait for T/2;
147      PCWrite <= '1';
148      wait for T/2;
149      — ID/Bra Calc
150      PCWrite <= '0';
151      MemRead <= '0';
152      IRWrite <= '0';
153      ALUSrcA <= ASA_PC;
154      ALUSrcB <= ASB_SEXTS;
155      PCSrc <= PS_PCINC;
156      ALUOp <= AOP_ADD;
157      wait for T;
158
159      — Memory Address Comp
160      ALUSrcA <= ASA_REG_A;
161      ALUSrcB <= ASB_SEXT;
162      ALUOp <= AOP_ADD;
163      wait for T;
164
165      — Memory Access
166      IorD <= IOD_ALUOUT;
167      wait for T/2;
168      MemWrite <= '1';
169      wait for T/2;
170
171
172      END PROCESS;
173
174 end architecture SW_Testbench_1;

```

Listing 19: SW\_Testbench